



FUNCTIONAL DESCRIPTION

The power supply uses a PIC12F1501 for implementing the proportional loop control. The algorithm for adjusting the output voltage and current is done in software, where the information about the output voltage and the load current (10-bit ADC channels) is used for controlling the closed loop. The circuit uses the NCO peripheral to generate a fixed on-time, variable frequency control signal for a buck converter. The “on time” is fixed to 2 μ s and the duty cycle is limited in firmware to about 90% at 450 kHz. The NCO frequency step is about 16 Hz using a 16 MHz clock source.

The control loop modifies the NCO frequency (essentially modifying duty cycle – fixed on-time, different period) to regulate the converter output. The decisions are made based on the ADC values read from the output voltage resistor divider and the output current shunt.

Since only one control loop is running for both voltage and current regulation, a special function decides on each update which of the two needs to be regulated. In normal operating conditions, the control loop tries to match the output voltage to the reference. If the output current goes over the limit, the loop tries to match the output current to the maximum-allowed value by reducing the output voltage. A special counter prevents erratic behavior when transitioning from one mode to the other.


APPLICATIONS

The power supply uses digital proportional control for regulating the output but the update rate is only 4 kHz. This makes it slow to respond to sudden load variations and input voltage changes. For this reason, output voltage is clamped by a very fast comparator-based, overvoltage protection mechanism.

On the other hand, a digital power supply has huge advantages. Output current and voltage can be modified during run-time by the application and complex algorithms like multi-step battery charging algorithms can be easily implemented. The peripheral configuration allows 15 bits of duty-cycle resolution for the transistor control signal, which enables very fine control of output voltage and current.

The main application areas of this power supply are battery chargers, LED drivers, thermoelectric cell drivers, programmable bias generators, and so on. With an accurate voltage reference, the circuit is more than adequate for charging sensitive Li-Ion batteries.

FIGURE 3: DUTY CYCLE vs. FREQUENCY USING FIXED ON-TIME (PF MODE)

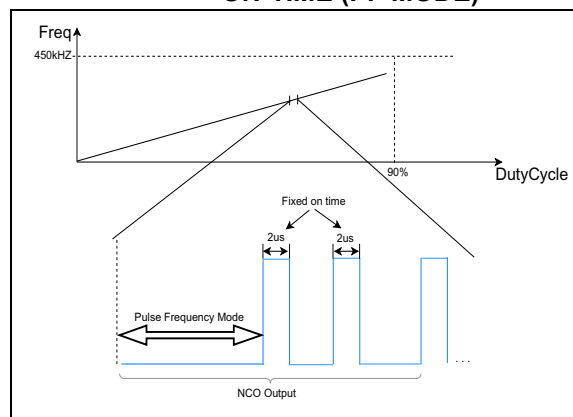

MCU PERIPHERAL CONFIGURATION DRAWING

The application only needs two analog channels (one for output voltage and the other one for current sense) for the loop control algorithm. The comparator input for the overvoltage protection is configured on the same pin as the output voltage ADC input.

At the run-time, the two programming pins (PGC and PGD) can be used for other purposes, if required. The configuration of the PIC12F1501 pins for implementing the proportional control loop application is listed in the following table (see [Table 2](#)):

**TABLE 2: PIC12F1501 PERIPHERAL
CONFIGURATION**

Pin No.	Name	Function
1	VDD	Supply voltage
2	RA5	NCO channel used for providing PWM signal for the proportional control loop
3	AN3	Analog input used for reading output voltage (VOUT) used in the feedback loop
4	RA3	Digital input – this input will provide start/stop functionality for the control loop algorithm
5	AN2	Analog input used for reading the current sense
6	PGC	Programming clock
7	PGD	Program data
8	VSS	Ground reference

SCOPE PLOTS OF KEY PARAMETERS

The following table (see [Table 3](#)) contains some characteristics of the charger obtained with an input of 14.3V and an output of 5V.

TABLE 3: POWER SUPPLY CHARACTERISTICS

Output Current (mA) ⁽²⁾	Sw. Frequency (kHz) ⁽³⁾	Efficiency (%) ⁽¹⁾
0	0.1-0.5	
50	11	78.0
100	22	81.3
250	56	84.6
500	108	86.4
1000	184	87.6
1200	184	88.1
1400	184	88.5
1600	184	88.8
1800	184	88.8
2000	180	88.5

Note 1: Efficiency is calculated including power loss on current shunt.

2: At 2A, the converter is running in current limiting mode.

3: PWM is fixed on-time (2 μ s) with variable frequency.

FIGURE 5: OPERATING FREQUENCY vs. LOAD CURRENT

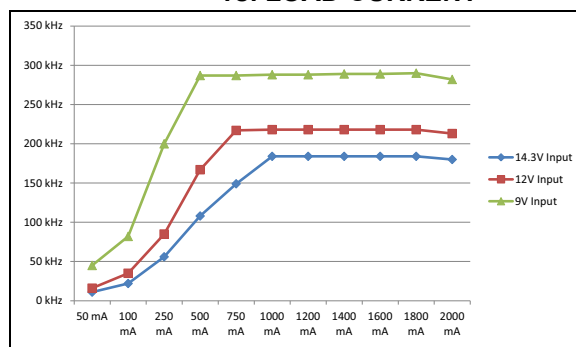


Figure 5 shows the converter operating frequency for 14.3V, 12V and 9V input at different output currents. Once the inductor current becomes continuous, the frequency/duty cycle changes very little, only to compensate for component power losses.

POWERING THE DEMONSTRATION HW

The board is powered from the input J1 connector with an input voltage between 8V and 16V.


The output voltage ($V_{OUT} = 5V$) is obtained at J2 connector and J4 connector (USB connector).

WHERE TO FIND THE CODE AND SCHEMATICS

The code can be downloaded from www.microchip.com.

For a better understanding of the implemented algorithm, please see the following flowchart diagram ([Figure 6](#)):

FIGURE 6: ALGORITHM FLOWCHART

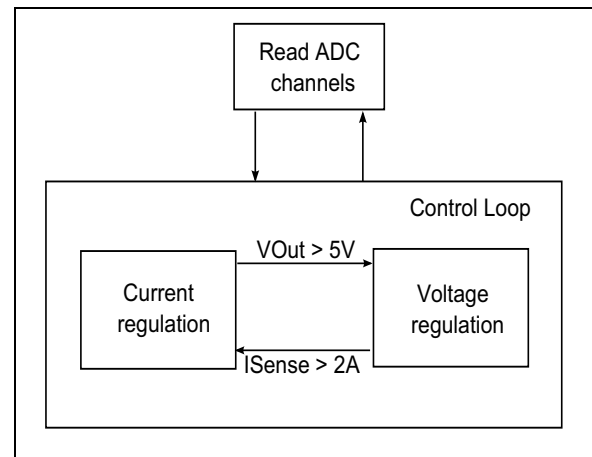


GLOSSARY

TABLE 4: ACRONYMS

PWM	Pulse-Width Modulation
ADC	Analog-to-Digital Converter
DAC	Digital-to-Analog Converter
NCO	Numerically Controlled Oscillator
PID	Proportional Integral Derivative
CWG	Complementary Waveform Generator

APPENDIX A:

FIGURE 7: SCHEMATIC

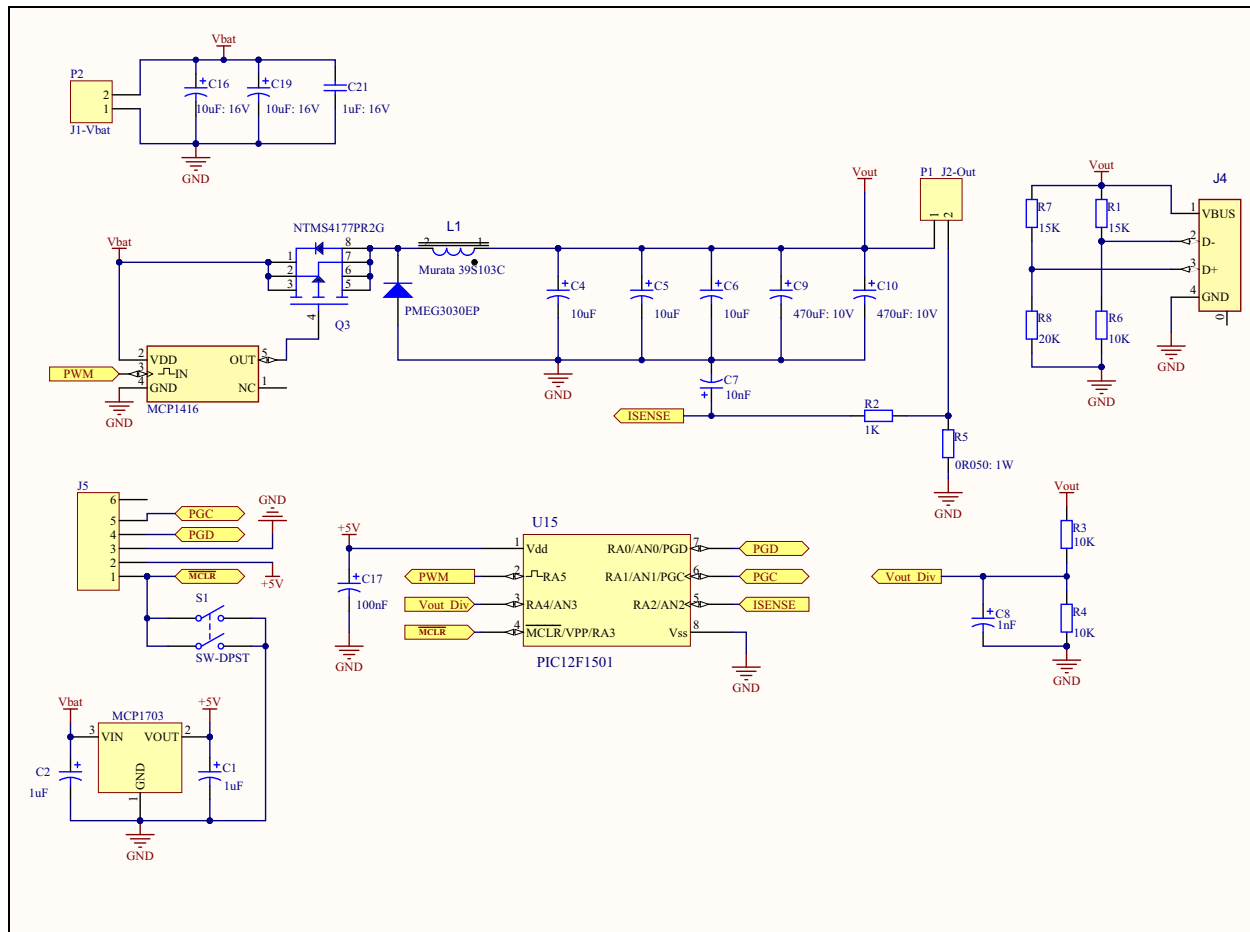

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, dsPIC, FlashFlex, KEELOQ, KEELOQ logo, MPLAB, PIC, PICmicro, PICSTART, PIC³² logo, rPIC, SST, SST Logo, SuperFlash and UNI/O are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

FilterLab, Hampshire, HI-TECH C, Linear Active Thermistor, MTP, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Silicon Storage Technology is a registered trademark of Microchip Technology Inc. in other countries.

Analog-for-the-Digital Age, Application Maestro, BodyCom, chipKIT, chipKIT logo, CodeGuard, dsPICDEM, dsPICDEM.net, dsPICworks, dsSPEAK, ECAN, ECONOMONITOR, FanSense, HI-TIDE, In-Circuit Serial Programming, ICSP, Mindi, MiWi, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, mTouch, Omniclient Code Generation, PICC, PICC-18, PICDEM, PICDEM.net, PICkit, PICTail, REAL ICE, rLAB, Select Mode, SQI, Serial Quad I/O, Total Endurance, TSHARC, UniWinDriver, WiperLock, ZENA and Z-Scale are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

GestIC and ULPP are registered trademarks of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies.

© 2013, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.



Printed on recycled paper.

ISBN: 9781620773741

QUALITY MANAGEMENT SYSTEM
CERTIFIED BY DNV
= ISO/TS 16949 =

Microchip received ISO/TS-16949:2009 certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona; Gresham, Oregon and design centers in California and India. The Company's quality system processes and procedures are for its PIC® MCUs and dsPIC® DSCs, KEELOQ® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.

Worldwide Sales and Service

AMERICAS

Corporate Office
2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support:
<http://www.microchip.com/support>
Web Address:
www.microchip.com

Atlanta
Duluth, GA
Tel: 678-957-9614
Fax: 678-957-1455

Boston
Westborough, MA
Tel: 774-760-0087
Fax: 774-760-0088

Chicago
Itasca, IL
Tel: 630-285-0071
Fax: 630-285-0075

Cleveland
Independence, OH
Tel: 216-447-0464
Fax: 216-447-0643

Dallas
Addison, TX
Tel: 972-818-7423
Fax: 972-818-2924

Detroit
Farmington Hills, MI
Tel: 248-538-2250
Fax: 248-538-2260

Indianapolis
Noblesville, IN
Tel: 317-773-8323
Fax: 317-773-5453

Los Angeles
Mission Viejo, CA
Tel: 949-462-9523
Fax: 949-462-9608

Santa Clara
Santa Clara, CA
Tel: 408-961-6444
Fax: 408-961-6445

Toronto
Mississauga, Ontario,
Canada
Tel: 905-673-0699
Fax: 905-673-6509

ASIA/PACIFIC

Asia Pacific Office
Suites 3707-14, 37th Floor
Tower 6, The Gateway
Harbour City, Kowloon
Hong Kong
Tel: 852-2401-1200
Fax: 852-2401-3431

Australia - Sydney
Tel: 61-2-9868-6733
Fax: 61-2-9868-6755

China - Beijing
Tel: 86-10-8569-7000
Fax: 86-10-8528-2104

China - Chengdu
Tel: 86-28-8665-5511
Fax: 86-28-8665-7889

China - Chongqing
Tel: 86-23-8980-9588
Fax: 86-23-8980-9500

China - Hangzhou
Tel: 86-571-2819-3187
Fax: 86-571-2819-3189

China - Hong Kong SAR
Tel: 852-2943-5100
Fax: 852-2401-3431

China - Nanjing
Tel: 86-25-8473-2460
Fax: 86-25-8473-2470

China - Qingdao
Tel: 86-532-8502-7355
Fax: 86-532-8502-7205

China - Shanghai
Tel: 86-21-5407-5533
Fax: 86-21-5407-5066

China - Shenyang
Tel: 86-24-2334-2829
Fax: 86-24-2334-2393

China - Shenzhen
Tel: 86-755-8864-2200
Fax: 86-755-8203-1760

China - Wuhan
Tel: 86-27-5980-5300
Fax: 86-27-5980-5118

China - Xian
Tel: 86-29-8833-7252
Fax: 86-29-8833-7256

China - Xiamen
Tel: 86-592-2388138
Fax: 86-592-2388130

China - Zhuhai
Tel: 86-756-3210040
Fax: 86-756-3210049

ASIA/PACIFIC

India - Bangalore
Tel: 91-80-3090-4444
Fax: 91-80-3090-4123

India - New Delhi
Tel: 91-11-4160-8631
Fax: 91-11-4160-8632

India - Pune
Tel: 91-20-2566-1512
Fax: 91-20-2566-1513

Japan - Osaka
Tel: 81-6-6152-7160
Fax: 81-6-6152-9310

Japan - Tokyo
Tel: 81-3-6880-3770
Fax: 81-3-6880-3771

Korea - Daegu
Tel: 82-53-744-4301
Fax: 82-53-744-4302

Korea - Seoul
Tel: 82-2-554-7200
Fax: 82-2-558-5932 or
82-2-558-5934

Malaysia - Kuala Lumpur
Tel: 60-3-6201-9857
Fax: 60-3-6201-9859

Malaysia - Penang
Tel: 60-4-227-8870
Fax: 60-4-227-4068

Philippines - Manila
Tel: 63-2-634-9065
Fax: 63-2-634-9069

Singapore
Tel: 65-6334-8870
Fax: 65-6334-8850

Taiwan - Hsin Chu
Tel: 886-3-5778-366
Fax: 886-3-5770-955

Taiwan - Kaohsiung
Tel: 886-7-213-7828
Fax: 886-7-330-9305

Taiwan - Taipei
Tel: 886-2-2508-8600
Fax: 886-2-2508-0102

Thailand - Bangkok
Tel: 66-2-694-1351
Fax: 66-2-694-1350

EUROPE

Austria - Wels
Tel: 43-7242-2244-39
Fax: 43-7242-2244-393

Denmark - Copenhagen
Tel: 45-4450-2828
Fax: 45-4485-2829

France - Paris
Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany - Munich
Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Italy - Milan
Tel: 39-0331-742611
Fax: 39-0331-466781

Netherlands - Drunen
Tel: 31-416-690399
Fax: 31-416-690340

Spain - Madrid
Tel: 34-91-708-08-90
Fax: 34-91-708-08-91

UK - Wokingham
Tel: 44-118-921-5869
Fax: 44-118-921-5820