

Differential Clock Translation

Author: Microchip Engineering Staff
Microchip Technology Inc.

INTRODUCTION

Considering that each available clock logic type (LVPECL, HCSL, CML, and LVDS) operates with a different common-mode voltage and swing level than the next (see Table 1), it is necessary to design clock logic translation between the driver side and receiver side for any given system design. This application note details how to translate one differential clock into other types of differential logics by adding attenuation resistors and bias circuits between them to attenuate the swing level and re-bias the common-mode for the input of the receiver.

TABLE 1: COMMON-MODE VOLTAGE AND SWING LEVELS OF DIFFERENT CLOCK LOGIC TYPES

Spec.	LVPECL	LVDS	CML ⁽¹⁾	HCSL
V_{CM}	$V_{CC} - 1.4V$	1.2V	$V_{CC} - 0.2V$	350 mV
V_{SWING_SE}	800 mV	325 mV	400 mV	700 mV
V_{OH}	$V_{CC} - 1V$	1.3625V	V_{CC}	700 mV
V_{OL}	$V_{CC} - 1.8V$	1.0375V	$V_{CC} - 0.400V$	0V
Reference	V_{CC}	Ground	V_{CC}	Ground

Note 1: Terminated 50Ω to V_{CC} .

INPUT/OUTPUT STRUCTURE OF EACH DIFFERENTIAL CLOCK LOGIC

Prior to designing the logic translation circuit, an examination of the input/output structures of each logic type — LVPECL, HCSL, CML, and LVDS — is required as each logic type features a different common-mode voltage and swing level.

Low-Voltage, Positive-Reference, Emitter-Coupled Logic (LVPECL)

Low-voltage, positive-referenced, emitter-coupled logic (LVPECL) originates from emitter-coupled logic (ECL), adopting a positive power supply.

The LVPECL input is a current-switching differential pair with high input impedance (see Figure 1). The input common-mode voltage should be approximately $V_{CC} - 1.3V$ for the purpose of having operating headroom, either from internal self-biasing or external biasing.

The LVPECL output consists of a differential pair amplifier which drives a pair of emitter followers (or open emitters) as illustrated in Figure 1. The output emitter followers should operate in the “active” region with DC current at all times. The output pins of OUT+ and OUT– are typically connected to differential transmission lines ($Z_0 = 100\Omega$) or a single-ended transmission line ($Z_0 = 50\Omega$) for impedance matching. The proper termination for LVPECL output is 50Ω to $V_{CC} - 2V$ and OUT+/OUT– will typically be $V_{CC} - 1.3V$, resulting in an approximate DC current flow of 14 mA.

Another way to terminate LVPECL output is to apply 142Ω to GND, which provides a DC-biasing for LVPECL output and a DC current path to GND. Because the LVPECL output common-mode is at $V_{CC} - 1.3V$, the DC-biasing resistor can be selected by assuming a DC current of 14 mA ($R = V_{CC} - 1.3V / 14 \text{ mA}$), resulting in $R = 142\Omega$ (150Ω also works) for $V_{CC} - 3.3V$.

 


FIGURE 1: LVPECL Input/Output Structure.

Low-Voltage Differential Signaling (LVDS)

Low-voltage differential signaling (LVDS) input requires a 100Ω termination resistor across the pins of IN+ and IN– with a common-mode voltage of approximately 1.2V (see Figure 2). If the 100Ω termination is not included on-chip, it must be included on the printed circuit board (PCB).

The LVDS output driver consists of a 3.5 mA current source which is connected to differential outputs through a switching network. The output pins of OUT+ and OUT– are typically connecting to differential trans-

mission lines ($Z_0 = 100\Omega$) or a single-ended transmission line ($Z_0 = 50\Omega$) for impedance matching, which are terminated with a 100Ω resistor across the receiver inputs, resulting in 350 mV swing for LVDS logic (Figure 2).

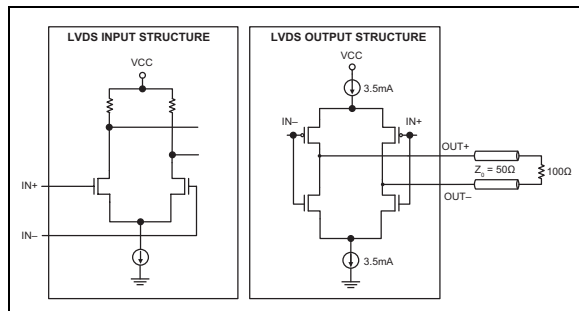


FIGURE 2: LVDS Input/Output Structure.

Current-Mode Logic (CML)

Most current-mode logic (CML) input structures have a 50Ω resistor to V_{CC} on-chip (see Figure 3). If not, then one must be applied to V_{DD} on both inputs of IN+ and IN- on the PCB. The input transistors are emitter followers which drive a differential-pair amplifier.

The CML output consists of a differential pair of common-emitter transistors with 50Ω collector resistors as the CML output structure illustrated in Figure 3 shows. The outputs of OUT+ and OUT- are typically connecting to differential transmission lines ($Z_0 = 100\Omega$) or a single-ended transmission line ($Z_0 = 50\Omega$) for impedance matching (Figure 3). The signal swing is provided by switching the current in a common-emitter differential BJT. Assuming the current source is 16 mA (typical) and the CML output is loaded with a 50Ω resistor that is pulled-up to V_{CC} , this will result in an output voltage swing from V_{CC} to $V_{CC} - 0.4V$ with a common-mode voltage ($V_{CC} - 0.2V$).

 


FIGURE 3: CML Input/Output Structure.

High-Speed Current-Steering Logic (HCSL)

The high-speed current-steering logic (HCSL) input requires the single-ended swing of 700 mV on both input pins of IN+ and IN- with a common-mode voltage of approximately 350 mV (see Figure 4).

A typical HCSL driver is a differential logic with open-source outputs, where each of the output pins switches between 0 and 14 mA. When one output pin is low (0), the other is high (driving 14 mA). The output pins of OUT+ and OUT- are typically connecting to differential transmission lines ($Z_0 = 100\Omega$) or a single-ended transmission line ($Z_0 = 50\Omega$), which requires an external termination resistor (50Ω to GND), resulting in a 700 mV swing level for HCSL input structures (Figure 4).

 


FIGURE 4: HCSL Input/Output Structure.

LVPECL-TO-CML TRANSLATION

As shown in Figure 5, placing a 150Ω resistor to GND at LVPECL driver output is essential for the open emitter to provide the DC-biasing as well as a DC current path to GND. In order to attenuate the 800 mV LVPECL swing to 400 mV CML swing, place a 50Ω attenuating resistor (R_A) after the 150Ω resistor to attenuate half of the LVPECL swing level. Additionally, self-biasing inside the CML receiver input must be confirmed. If the self-biasing at the input of CML is not present, a 50Ω termination resistor to V_{CC} must be placed on the PCB for CML biasing and transmission line termination.

Microchip's ultra-low-jitter crystal oscillators and clock generators (i.e., MX55, MX57, SM802xxx, SM803xxx, MX85xxx) can provide <0.3 ps RMS phase jitter with any type of output logics, except CML logic. With the below translation circuit, it is easy to achieve CML output from LVPECL logic.

 


FIGURE 5: LVPECL-to-CML Translation.

LVPECL-TO-LVDS TRANSLATION

Placing a 150Ω resistor to GND at LVPECL driver output is essential for the open emitter to provide the DC-biasing as well as a DC current path to GND (Figure 6). In order to attenuate the 800 mV LVPECL swing to a 325 mV LVDS swing, a 70Ω attenuating resistor must be applied after the 150Ω resistor. A 10 nF AC-coupled capacitor should be placed in front of the LVDS receiver to block DC level coming from the LVPECL driver. After the AC-coupled capacitor, re-biasing is required for the LVDS input and can be done by placing 8.7 kΩ resistor to 3.3V and 5 kΩ resistor to GND to achieve 1.2V DC level for the input common-mode of LVDS receiver. If the LVDS receiver already has integrated a 100Ω resistor across the differential input pins, the external 100Ω resistor is not required.

When Microchip's LVPECL fanout buffers (i.e., SY89831) have been qualified and adopted by customers—but some of the outputs require LVDS logics for the following receivers—this LVPECL-to-LVDS translation circuit is very helpful to achieve the target.

 


FIGURE 6: LVPECL-to-LVDS Translation.

LVPECL-TO-HCSL TRANSLATION

As shown in Figure 7, placing a 150Ω resistor to GND at LVPECL driver output is essential for the open emitter to provide the DC-biasing as well as a DC current path to GND. In order to attenuate an 800 mV LVPECL swing to a 700 mV HCSL swing, an attenuating resistor ($R_A = 8\Omega$) must be placed after the 150Ω resistor. A 10 nF AC-coupled capacitor should be placed in front of the HCSL receiver to block DC level coming from the LVPECL driver. After the AC-coupled capacitor is

placed, re-biasing is required for the HCSL input and can be done by placing 470Ω resistor to 3.3V and 56Ω resistor to GND to achieve 350 mV DC level for the input common-mode of HCSL receiver.

When Microchip's LVPECL fanout buffers (i.e., SY89831) have been qualified and adopted by customers—but some of the outputs require HCSL logics for the following receivers—this LVPECL-to-HCSL translation circuit is very helpful to achieve the target.

 


FIGURE 7: LVPECL-to-HCSL Translation.

HCSL-TO-LVDS TRANSLATION

In Figure 8, each of HCSL output pins switches between 0 and 14 mA. When one output pin is low (0), the other is high (driving 14 mA). The equivalent loading for HCSL driver is 48Ω parallel to 50Ω, which equates 23.11Ω. The swing level on the LVDS input is $14 \text{ mA} \times 23.11\Omega = 323 \text{ mV}$. A 10 nF AC-coupled capacitor should be placed in front of the LVDS receiver to block DC level coming from the HCSL driver. After the AC-coupled capacitor is placed, re-biasing is required for the LVDS input and can be done by placing 8.7 kΩ resistor to 3.3V and 5 kΩ resistor to GND to achieve 1.2V DC level for the input common-mode of LVDS Receiver. If the LVDS receiver already has integrated a 100Ω resistor across the differential input pins, the external 100Ω resistor is not required.

When Microchip's HCSL fanout buffers (i.e., SY75576L, SY75578L) have been qualified and adopted by customers—but some of the outputs require LVDS logics for the following receivers—this HCSL-to-LVDS translation circuit is very helpful to achieve the target.

 


FIGURE 8: HCSL-to-LVDS Translation.

HCSL-TO-CML TRANSLATION

In [Figure 9](#), each of HCSL output pins switches between 0 and 14 mA. When one output pin is low (0), the other is high (driving 14 mA). The equivalent loading for HCSL driver is 68Ω parallel to 50Ω , which equates 28.81Ω . The swing level on the CML input is $14\text{ mA} \times 28.81\Omega = 403\text{ mV}$. A 10 nF AC-coupled capacitor should be placed in front of the CML receiver to block DC level coming from the HCSL driver. Additionally, self-biasing inside the CML receiver input must be confirmed. If the self-biasing at the input of CML is not present, a 50Ω termination resistor to V_{CC} must be placed on the PCB for CML biasing and transmission line termination.

Microchip's ultra-low-jitter crystal oscillators and clock generators (i.e., MX55, MX57, SM802xxx, SM803xxx, MX85xxx) can provide $<0.3\text{ ps}$ RMS phase jitter with any type of output logics, except CML logic. With the translation circuit below, it is easy to achieve CML output from HCSL logic.

 


FIGURE 9: HCSL-to-CML Translation.

LVDS-TO-CML TRANSLATION

LVDS output drives a $\pm 3.5\text{ mA}$ current through the termination of 100Ω resistor, resulting in a 350 mV swing level in front of the CML receiver ([Figure 10](#)). Confirmation that the CML receivers are capable of receiving a 350 mV swing is required because the standard swing of CML is 400 mV . Additionally, self-biasing inside the CML receiver input must also be confirmed. If the self-biasing at the input of CML is not present, a 50Ω termination resistor to V_{CC} must be placed on the PCB for CML biasing and transmission line termination.

Microchip's ultra-low-jitter crystal oscillators and clock generators (i.e., MX55, MX57, SM802xxx, SM803xxx, MX85xxx) can provide $<0.3\text{ ps}$ RMS phase jitter with any type of output logics, except CML logic. With the below translation circuit, it is easy to achieve CML output from LVDS logic.

 


FIGURE 10: LVDS-to-CML Translation.

SUMMARY

This application note presents how to translate different clock logics. With the proper signal level attenuation and self-biasing circuit in front of the receiver side, a translation circuit can be easily achieved with fewer external components.

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights unless otherwise stated.

Microchip received ISO/TS-16949:2009 certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona; Gresham, Oregon and design centers in California and India. The Company's quality system processes and procedures are for its PIC® MCUs and dsPIC® DSCs, KEELoc® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.

QUALITY MANAGEMENT SYSTEM
CERTIFIED BY DNV
== ISO/TS 16949 ==

Trademarks

The Microchip name and logo, the Microchip logo, AnyRate, dsPIC, FlashFlex, flexPWR, Helder, JukeBlox, KeeLoq, KeeLoq logo, Klear, LANCheck, LINK MD, MediaLB, MOST, MOST logo, MPLAB, OptoLyzer, PIC, PICSTART, PIC32 logo, RightTouch, SpyNIC, SST, SST Logo, SuperFlash and UNI/O are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

ClockWorks, The Embedded Control Solutions Company, ETHERSYNCH, Hyper Speed Control, HyperLight Load, IntelliMOS, mTouch, Precision Edge, and QUIET-WIRE are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, Any Capacitor, AnyIn, AnyOut, BodyCom, chipKIT, chipKIT logo, CodeGuard, dsPICDEM, dsPICDEM.net, Dynamic Average Matching, DAM, ECAN, EtherGREEN, In-Circuit Serial Programming, ICSP, Inter-Chip Connectivity, JitterBlocker, KlearNet, KlearNet logo, MiWi, motorBench, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, MultiTRAK, NetDetach, Omniscient Code Generation, PICDEM, PICDEM.net, PICkit, PICtail, PureSilicon, RightTouch logo, REAL ICE, Ripple Blocker, Serial Quad I/O, SQL, SuperSwitcher, SuperSwitcher II, Total Endurance, TSHARC, USBCheck, VariSense, ViewSpan, WiperLock, Wireless DNA, and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

Silicon Storage Technology is a registered trademark of Microchip Technology Inc. in other countries.

GestIC is a registered trademarks of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies.

© 2016, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

ISBN: 978-1-5224-0718-8

Worldwide Sales and Service

AMERICAS

Corporate Office
2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support:
<http://www.microchip.com/support>
Web Address:
www.microchip.com

Atlanta
Duluth, GA
Tel: 678-957-9614
Fax: 678-957-1455

Austin, TX
Tel: 512-257-3370

Boston
Westborough, MA
Tel: 774-760-0087
Fax: 774-760-0088

Chicago
Itasca, IL
Tel: 630-285-0071
Fax: 630-285-0075

Cleveland
Independence, OH
Tel: 216-447-0464
Fax: 216-447-0643

Dallas
Addison, TX
Tel: 972-818-7423
Fax: 972-818-2924

Detroit
Novi, MI
Tel: 248-848-4000

Houston, TX
Tel: 281-894-5983

Indianapolis
Noblesville, IN
Tel: 317-773-8323
Fax: 317-773-5453

Los Angeles
Mission Viejo, CA
Tel: 949-462-9523
Fax: 949-462-9608

New York, NY
Tel: 631-435-6000

San Jose, CA
Tel: 408-735-9110

Canada - Toronto
Tel: 905-673-0699
Fax: 905-673-6509

ASIA/PACIFIC

Asia Pacific Office
Suites 3707-14, 37th Floor
Tower 6, The Gateway
Harbour City, Kowloon

Hong Kong
Tel: 852-2943-5100
Fax: 852-2401-3431

Australia - Sydney
Tel: 61-2-9868-6733
Fax: 61-2-9868-6755

China - Beijing
Tel: 86-10-8569-7000
Fax: 86-10-8528-2104

China - Chengdu
Tel: 86-28-8665-5511
Fax: 86-28-8665-7889

China - Chongqing
Tel: 86-23-8980-9588
Fax: 86-23-8980-9500

China - Dongguan
Tel: 86-769-8702-9880

China - Guangzhou
Tel: 86-20-8755-8029

China - Hangzhou
Tel: 86-571-8792-8115
Fax: 86-571-8792-8116

China - Hong Kong SAR
Tel: 852-2943-5100
Fax: 852-2401-3431

China - Nanjing
Tel: 86-25-8473-2460
Fax: 86-25-8473-2470

China - Qingdao
Tel: 86-532-8502-7355
Fax: 86-532-8502-7205

China - Shanghai
Tel: 86-21-5407-5533
Fax: 86-21-5407-5066

China - Shenyang
Tel: 86-24-2334-2829
Fax: 86-24-2334-2393

China - Shenzhen
Tel: 86-755-8864-2200
Fax: 86-755-8203-1760

China - Wuhan
Tel: 86-27-5980-5300
Fax: 86-27-5980-5118

China - Xian
Tel: 86-29-8833-7252
Fax: 86-29-8833-7256

ASIA/PACIFIC

China - Xiamen
Tel: 86-592-2388138
Fax: 86-592-2388130

China - Zhuhai
Tel: 86-756-3210040
Fax: 86-756-3210049

India - Bangalore
Tel: 91-80-3090-4444
Fax: 91-80-3090-4123

India - New Delhi
Tel: 91-11-4160-8631
Fax: 91-11-4160-8632

India - Pune
Tel: 91-20-3019-1500

Japan - Osaka
Tel: 81-6-6152-7160
Fax: 81-6-6152-9310

Japan - Tokyo
Tel: 81-3-6880-3770
Fax: 81-3-6880-3771

Korea - Daegu
Tel: 82-53-744-4301
Fax: 82-53-744-4302

Korea - Seoul
Tel: 82-2-554-7200
Fax: 82-2-558-5932 or
82-2-558-5934

Malaysia - Kuala Lumpur
Tel: 60-3-6201-9857
Fax: 60-3-6201-9859

Malaysia - Penang
Tel: 60-4-227-8870
Fax: 60-4-227-4068

Philippines - Manila
Tel: 63-2-634-9065
Fax: 63-2-634-9069

Singapore
Tel: 65-6334-8870
Fax: 65-6334-8850

Taiwan - Hsin Chu
Tel: 886-3-5778-366
Fax: 886-3-5770-955

Taiwan - Kaohsiung
Tel: 886-7-213-7828

Taiwan - Taipei
Tel: 886-2-2508-8600
Fax: 886-2-2508-0102

Thailand - Bangkok
Tel: 66-2-694-1351
Fax: 66-2-694-1350

EUROPE

Austria - Wels
Tel: 43-7242-2244-39
Fax: 43-7242-2244-393

Denmark - Copenhagen
Tel: 45-4450-2828
Fax: 45-4485-2829

France - Paris
Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany - Dusseldorf
Tel: 49-2129-3766400

Germany - Karlsruhe
Tel: 49-721-625370

Germany - Munich
Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Italy - Milan
Tel: 39-0331-742611
Fax: 39-0331-466781

Italy - Venice
Tel: 39-049-7625286

Netherlands - Drunen
Tel: 31-416-690399
Fax: 31-416-690340

Poland - Warsaw
Tel: 48-22-3325737

Spain - Madrid
Tel: 34-91-708-08-90
Fax: 34-91-708-08-91

Sweden - Stockholm
Tel: 46-8-5090-4654

UK - Wokingham
Tel: 44-118-921-5800
Fax: 44-118-921-5820