



# MCP16311/2 High Efficiency Buck-Boost Converter

Author: Andrei Radulescu

Microchip Technology Inc.

## INTRODUCTION

This Technical Brief proposes a high-efficiency buck-boost converter design which is implemented using the simple 30V input MCP16311/2 synchronous step-down switching regulator with a typical application depicted in Figure 1. There are many buck-boost converter designs available in the literature, but most of them suffer from low-efficiency, which is mainly caused by the utilization of four switches that operate alternately. This application not only demonstrates that the MCP16311/2 can be used in a step-down/step-up converter, but also comprises a method of improving the converter's efficiency while enhancing the output current capabilities in some conditions.

The proposed method consists in providing a buck-only operation as shown in Figure 2. This is described in detail in the **Mode of Operation** section.

The MCP16311/2 is a compact, high-efficiency, fixed frequency, synchronous step-down DC-DC converter in an 8-pin MSOP and 2 mm x 3 mm TDFN package that operates from input voltage sources up to 30V. Integrated features include a high-side and a low-side switch, fixed frequency peak current mode control, internal compensation, peak current limit and overtemperature protection. The MCP16311/2 provides all of the active functions for local DC-DC conversion with fast transient response and accurate regulation.

MCP16311/2 switching regulator's high-efficiency is achieved by integrating the current-limited, low-resistance, high-speed, high-side and low-side switches and associated drive circuitry. The MCP16311 is capable of running in Pulse Frequency Modulation/ Pulse Width Modulation (PFM/PWM) mode. It switches in PFM mode for light load conditions and for large Buck conversion ratios. This results in a higher efficiency over all load ranges. The MCP16312 runs in PWM-only mode and is recommended for noise-sensitive applications.

The MCP16311/2 device family can supply up to 1A of continuous current while regulating the output voltage from 2V to 12V. An integrated high-performance peak current mode architecture keeps the output voltage

tightly regulated, even during input voltage steps and output current transient conditions which are common in power systems.

The EN input is used to turn the device on and off. While off, only a few micro amps of current are drawn from the input.

Output voltage is set with an external resistive divider. The MCP16311/2 is offered in small MSOP-8 and 2 mm x 3 mm TDFN surface mount packages.

#### **DEVICE FEATURES**

- Up to 95% Efficiency
- Input Voltage Range: 4.4V to 30V
- · 1A Output Current Capability
- Qualification: AEC-Q100 Rev. G, Grade 1 (-40°C to +125°C)
- Integrated N-Channel High-Side and Low-Side Switches:
  - 170 mΩ Low Side
  - 300 mΩ High Side
- Stable Reference Voltage: 0.8V
- Automatic PFM/PWM Operation (MCP16311):
  - PFM Operation Disabled (MCP16312)
  - PWM Operation: 500 kHz
- Low Device Shutdown Current: 3 μA typical
- Low Device Quiescent Current: 44 μA (Non-switching, PFM Mode)
- · Internal Compensation
- Internal Soft-Start: 300 µs (EN Low-to-High)
- · Peak Current Mode Control
- Cycle-by-Cycle Peak Current Limit
- Undervoltage Lockout (UVLO)
  - 4.1V typical to start
  - 3.6V typical to stop
- · Thermal Shutdown:
  - +150°C
  - +25°C Hysteresis

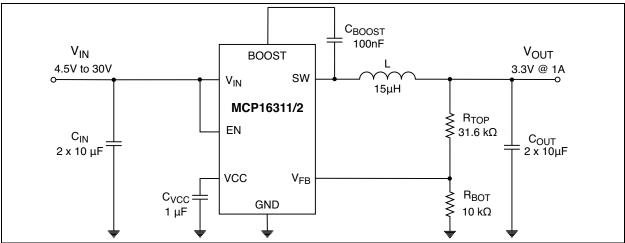


FIGURE 1: MCP16311/2 Typical Step-Down (Buck) Application.

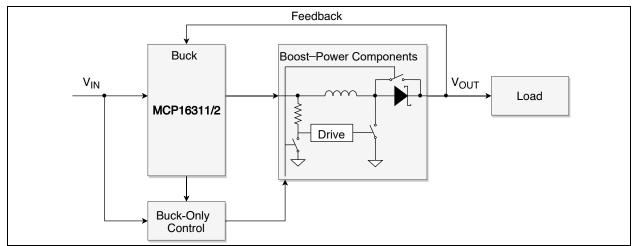


FIGURE 2: MCP16311/2 High Efficiency Buck-Boost Converter Simplified Block Diagram.

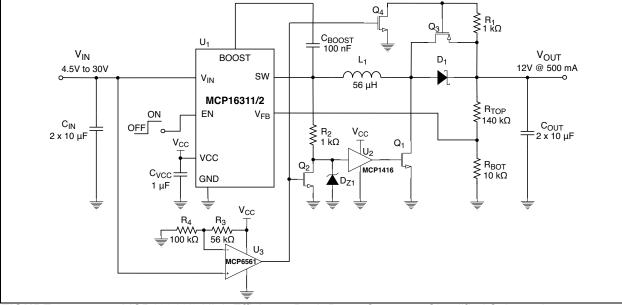


FIGURE 3: MCP16311/2 High Efficiency Buck-Boost Converter Simplified Schematic.

#### MODE OF OPERATION

The proposed solution is a conventional noninverting buck-boost converter which uses a single inductor (Figure 3), and has an additional MOSFET ( $Q_1$ ) and an additional diode ( $D_1$ ), compared to a classic inverting buck-boost or a step-down converter. By turning the internal high-side switch together with  $Q_1$  on and off simultaneously, the converter operates in buck-boost mode. The ideal waveforms of a noninverting buck-boost converter operating in buck-boost mode and Continuous Conduction Mode (CCM) are shown in Figure 4.

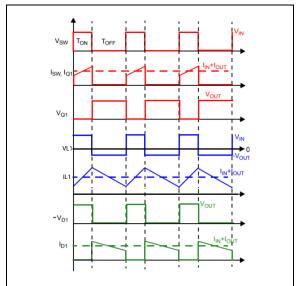


FIGURE 4: Noninverting Buck-Boost Converter Waveforms in CCM.

With regard to the ratings, both the internal high-side and low-side switches see a voltage stress of  $V_{IN},$  while  $Q_1$  and  $D_1$  see a voltage stress of  $V_{OUT}.$  The internal high-side and low-side switches, together with  $Q_1,\,D_1$  and  $L_1,\,$  all see a current stress of  $I_{IN}+I_{OUT},\,$  with inductor ripple current neglected. The relatively large number of power devices and high-current stress in buck-boost mode prevent the converter from being efficient.

The proposed noninverting buck-boost converter is a cascaded combination of a Buck converter followed by a Boost converter, both sharing the same inductor. The internal high-side switch and  $Q_1$  have identical gate-control signals. In order to increase the converter efficiency (Figure 5) and maximum output current capabilities (Figure 6), a few additional components are needed ( $Q_2$ ,  $Q_3$  and  $U_3$ ) and represent a slight increase in complexity. The mode of operation for the proposed circuit is described in the following paragraphs.

When the input voltage is greater than the output voltage ( $V_{\text{IN}} > V_{\text{OUT}}$ ), the output of the U<sub>3</sub> comparator goes from low to high and turns on Q<sub>2</sub> and Q<sub>3</sub> switches, in order to disable the Pulse-Width Modulation (PWM) signal for the main switch of the Boost leg and to bypass its rectifier (Schottky diode). As a result, Q<sub>1</sub> and D<sub>1</sub> are off and the circuit operates as a Buck converter. The comparator (U<sub>3</sub>) has a hysteresis adjusted to about 400 mV to avoid instability when the input voltage is very close to the threshold value.


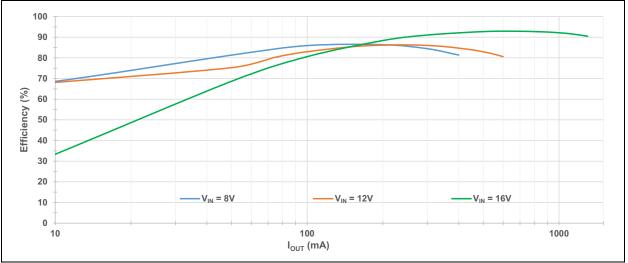


FIGURE 5: MCP16311/2 High Efficiency Buck-Boost Converter Efficiency Plot vs. Output Current for 12V V<sub>OUT</sub>.

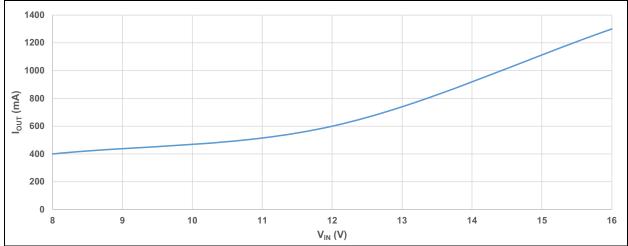

**FIGURE 6:** MCP16311/2 High Efficiency Buck-Boost Converter Maximum Output Current vs. Input Voltage for 12V V<sub>OUT</sub>.

# NONINVERTING BUCK-BOOST CONVERTER DESIGN STAGE

In order to calculate the noninverting buck-boost converter application parameters and inductor's value for Continuous Conduction Mode operation, Equations 1 to 5 can be used.

#### **EQUATION 1: DUTY CYCLE**

$$D = \frac{V_{OUT} + V_D}{V_{IN} + V_{OUT} + V_D}$$

#### **EQUATION 2: MAXIMUM DUTY CYCLE**

$$D_{max} = \frac{V_{OUT} + V_D}{V_{INmin} + V_{OUT} + V_D}$$

Note 1: V<sub>D</sub> represents the voltage drop on D<sub>1</sub> diode

The duty cycle of the noninverting buck-boost converter can be calculated using the equations above; at minimum input voltage ( $V_{INmin}$ ), the duty cycle has the maximum value, while at maximum input voltage ( $V_{INmax}$ ), the duty cycle has the minimum value. For the noninverting buck-boost converter, the DC current flowing through  $L_1$  is the sum of the input current and output current.

# EQUATION 3: INDUCTOR RIPPLE CURRENT

$$I_{Lp-p} = (I_{IN} + I_{OUT}) \times k$$

**Note 1:** k takes values between 0.2 to 0.4

2: k represents a percentage of the inductor current The inductor ripple current represents a percentage of the DC current; depending on the application, this percentage is usually chosen between 20% and 40%. The higher the ripple (coefficient k is higher), the lower the inductor value. Therefore, output current capabilities will be lower, as the current ripple will reach the peak current limitation sooner.

For lower k coefficient values, the inductance will be higher; the output current will increase as the ripple will decrease, requiring more load to hit the current limit. As a result of higher output current, the power dissipation of the device needs to be taken into consideration; the converter may enter thermal shutdown before reaching the peak current limit. Eventually, requirements of the application will determine the acceptable inductor current ripple range. However, because MCP16311/2 is a peak current mode control converter, it requires a significant inductor current ripple, in order to provide the best transient response. Usually, a k = 30% is a good trade-off between output current capabilities and dynamic response.

The inductor's peak current is dependent on the following parameters, as shown in Equation 4:

- · Converter's input current
- · Converter's output current
- The inductor current ripple which is designed to meet the application requirements

# **EQUATION 4: INDUCTOR PEAK CURRENT**

$$I_{Lpeak} = I_{IN} + I_{OUT} + \frac{I_{Lp-p}}{2}$$

During the design phase, the efficiency of the converter is estimated, in order to simplify all the calculations. The real application results may differ to a small extent, because they are influenced by the component/system tolerances and accuracy of the estimated parameters.

The value of the inductor can be calculated using Equation 5.

#### **EQUATION 5: INDUCTOR VALUE**

$$L = \frac{V_{IN} \times D}{I_{Lp-p} \times f_{SW}}$$

**Note 1:**  $f_{SW}$  represents the switching frequency

#### **High Inductor Current Ripple**

- · Advantages:
  - Lower inductor value required, lowering application's necessary board space, thus reducing overall costs
  - Better dynamic response
- · Drawbacks:
  - Lower output current capabilities
  - Increased EMI (electromagnetic interference), therefore requiring additional output filtering

## **Low Inductor Current Ripple**

- · Advantages:
  - Higher output current capabilities
  - Decreased EMI
- · Drawbacks:
  - Bigger inductor value/package (size)

One possible implementation of the proposed buck-boost converter Printed Circuit Board (PCB) assembly is shown in Figure 7.

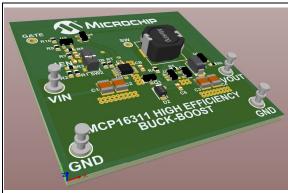


FIGURE 7: MCP16311/2 High Efficiency Buck-Boost Assembly.

### **CONCLUSIONS**

When a step-down/step-up DC/DC converter solution is needed for an application, some engineers might be reluctant to choose the buck-boost topology, knowing that it might have limited output current capabilities and low efficiency. This technical brief proposes a solution to overcome these problems, which is represented by a noninverting buck-boost converter designed using the MCP16311/2 synchronous step-down switching regulator. With just a few additional components, (compared to a typical noninverting buck-boost converter) the overall efficiency, as well as the output current capabilities are improved.

### **REFERENCES**

- MCP16311/2 Data Sheet "30V Input, 1A Output, High-Efficiency, Integrated Synchronous Switch Step-Down Regulator" (DS20005255)
- AN2102 "Designing Applications with MCP16331 High-Input Voltage Buck Converter" (DS00002102)

# **TB3277**

NOTES:

#### Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specifications contained in their particular Microchip Data Sheet.
- · Microchip believes that its family of products is secure when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods being used in attempts to breach the code protection features of the Microchip devices. We believe that these methods require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Attempts to breach these code protection features, most likely, cannot be accomplished without violating Microchip's intellectual property rights.
- Microchip is willing to work with any customer who is concerned about the integrity of its code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of its code. Code protection does not mean that we are guaranteeing the product is "unbreakable." Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication is provided for the sole purpose of designing with and using Microchip products. Information regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications.

THIS INFORMATION IS PROVIDED BY MICROCHIP "AS IS". MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION INCLUDING BUT NOT LIMITED TO ANY IMPLIED WARRANTIES OF NON-INFRINGEMENT, MERCHANTABILITY, AND FITNESS FOR A PARTICULAR PURPOSE OR WARRANTIES RELATED TO ITS CONDITION, QUALITY, OR PERFORMANCE.

IN NO EVENT WILL MICROCHIP BE LIABLE FOR ANY INDI-RECT, SPECIAL, PUNITIVE, INCIDENTAL OR CONSEQUEN-TIAL LOSS, DAMAGE, COST OR EXPENSE OF ANY KIND WHATSOEVER RELATED TO THE INFORMATION OR ITS USE, HOWEVER CAUSED, EVEN IF MICROCHIP HAS BEEN ADVISED OF THE POSSIBILITY OR THE DAMAGES ARE FORESEEABLE. TO THE FULLEST EXTENT ALLOWED BY LAW, MICROCHIP'S TOTAL LIABILITY ON ALL CLAIMS IN ANY WAY RELATED TO THE INFORMATION OR ITS USE WILL NOT EXCEED THE AMOUNT OF FEES, IF ANY, THAT YOU HAVE PAID DIRECTLY TO MICROCHIP FOR THE INFORMATION. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights unless otherwise stated.

For information regarding Microchip's Quality Management Systems,

#### **Trademarks**

The Microchip name and logo, the Microchip logo, Adaptec, AnyRate, AVR, AVR logo, AVR Freaks, BesTime, BitCloud, chipKIT, chipKIT logo, CryptoMemory, CryptoRF, dsPIC, FlashFlex, flexPWR, HELDO, IGLOO, JukeBlox, KeeLoq, Kleer, LANCheck, LinkMD, maXStylus, maXTouch, MediaLB, megaAVR, Microsemi, Microsemi logo, MOST, MOST logo, MPLAB, OptoLyzer, PackeTime, PIC, picoPower, PICSTART, PIC32 logo, PolarFire, Prochip Designer, QTouch, SAM-BA, SenGenuity, SpyNIC, SST, SST Logo, SuperFlash, Symmetricom, SyncServer, Tachyon, TempTrackr, TimeSource, tinyAVR, UNI/O, Vectron, and XMEGA are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

APT, ClockWorks, The Embedded Control Solutions Company, EtherSynch, FlashTec, Hyper Speed Control, HyperLight Load, IntelliMOS, Libero, motorBench, mTouch, Powermite 3, Precision Edge, ProASIC, ProASIC Plus, ProASIC Plus logo, Quiet-Wire, SmartFusion, SyncWorld, Temux, TimeCesium, TimeHub, TimePictra, TimeProvider, Vite, WinPath, and ZL are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Adjacent Key Suppression, AKS, Analog-for-the-Digital Age, Any Capacitor, AnyIn, AnyOut, BlueSky, BodyCom, CodeGuard, CryptoAuthentication, CryptoAutomotive, CryptoCompanion, CryptoController, dsPICDEM, dsPICDEM.net, Dynamic Average Matching, DAM, ECAN, EtherGREEN, In-Circuit Serial Programming, ICSP, INICnet, Inter-Chip Connectivity, JitterBlocker, KleerNet, KleerNet logo, memBrain, Mindi, MiWi, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, MultiTRAK, NetDetach, Omniscient Code Generation, PICDEM, PICDEM.net, PICkit, PICtail, PowerSmart, PureSilicon, QMatrix, REAL ICE, Ripple Blocker, SAM-ICE, Serial Quad I/O, SMART-I.S., SQI, SuperSwitcher, SuperSwitcher II, Total Endurance, TSHARC, USBCheck, VariSense, ViewSpan, WiperLock, Wireless DNA, and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

The Adaptec logo, Frequency on Demand, Silicon Storage Technology, and Symmcom are registered trademarks of Microchip Technology Inc. in other countries.

GestIC is a registered trademark of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies.

© 2020, Microchip Technology Incorporated, All Rights Reserved.

ISBN: 978-1-5224-6710-6

please visit www.microchip.com/quality



# **Worldwide Sales and Service**

#### **AMERICAS**

**Corporate Office** 2355 West Chandler Blvd. Chandler, AZ 85224-6199 Tel: 480-792-7200

Fax: 480-792-7277 **Technical Support:** 

http://www.microchip.com/ support

Web Address:

www.microchip.com Atlanta

Duluth, GA Tel: 678-957-9614 Fax: 678-957-1455

Austin, TX Tel: 512-257-3370

**Boston** 

Westborough, MA Tel: 774-760-0087 Fax: 774-760-0088

Chicago Itasca, IL

Tel: 630-285-0071 Fax: 630-285-0075

**Dallas** Addison, TX Tel: 972-818-7423 Fax: 972-818-2924

**Detroit** Novi, MI

Tel: 248-848-4000

Houston, TX Tel: 281-894-5983

Indianapolis Noblesville, IN Tel: 317-773-8323 Fax: 317-773-5453

Tel: 317-536-2380

Los Angeles Mission Viejo, CA Tel: 949-462-9523 Fax: 949-462-9608 Tel: 951-273-7800

Raleigh, NC Tel: 919-844-7510

New York, NY Tel: 631-435-6000

San Jose, CA Tel: 408-735-9110 Tel: 408-436-4270

Canada - Toronto Tel: 905-695-1980 Fax: 905-695-2078

#### ASIA/PACIFIC

Australia - Sydney Tel: 61-2-9868-6733

China - Beijing Tel: 86-10-8569-7000

China - Chengdu Tel: 86-28-8665-5511

China - Chongqing Tel: 86-23-8980-9588

China - Dongguan Tel: 86-769-8702-9880

China - Guangzhou Tel: 86-20-8755-8029

China - Hangzhou Tel: 86-571-8792-8115

China - Hong Kong SAR Tel: 852-2943-5100

China - Nanjing Tel: 86-25-8473-2460

China - Qingdao Tel: 86-532-8502-7355

China - Shanghai Tel: 86-21-3326-8000

China - Shenyang Tel: 86-24-2334-2829

China - Shenzhen Tel: 86-755-8864-2200

China - Suzhou Tel: 86-186-6233-1526

China - Wuhan

Tel: 86-27-5980-5300 China - Xian

Tel: 86-29-8833-7252 China - Xiamen

China - Zhuhai Tel: 86-756-3210040

Tel: 86-592-2388138

#### ASIA/PACIFIC

India - Bangalore Tel: 91-80-3090-4444

India - New Delhi Tel: 91-11-4160-8631

India - Pune Tel: 91-20-4121-0141

Japan - Osaka Tel: 81-6-6152-7160

Japan - Tokyo Tel: 81-3-6880- 3770

Korea - Daegu Tel: 82-53-744-4301

Korea - Seoul Tel: 82-2-554-7200

Malaysia - Kuala Lumpur Tel: 60-3-7651-7906

Malaysia - Penang Tel: 60-4-227-8870

Philippines - Manila Tel: 63-2-634-9065

Singapore Tel: 65-6334-8870

Taiwan - Hsin Chu Tel: 886-3-577-8366

Taiwan - Kaohsiung Tel: 886-7-213-7830

Taiwan - Taipei Tel: 886-2-2508-8600

Thailand - Bangkok Tel: 66-2-694-1351

Vietnam - Ho Chi Minh Tel: 84-28-5448-2100

#### **EUROPE**

Austria - Wels Tel: 43-7242-2244-39 Fax: 43-7242-2244-393

Denmark - Copenhagen Tel: 45-4485-5910 Fax: 45-4485-2829

Finland - Espoo Tel: 358-9-4520-820

France - Paris Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

Germany - Garching Tel: 49-8931-9700

Germany - Haan Tel: 49-2129-3766400

Germany - Heilbronn Tel: 49-7131-72400

Germany - Karlsruhe Tel: 49-721-625370

Germany - Munich Tel: 49-89-627-144-0 Fax: 49-89-627-144-44

Germany - Rosenheim Tel: 49-8031-354-560

Israel - Ra'anana Tel: 972-9-744-7705

Italy - Milan Tel: 39-0331-742611 Fax: 39-0331-466781

Italy - Padova Tel: 39-049-7625286

Netherlands - Drunen Tel: 31-416-690399 Fax: 31-416-690340

Norway - Trondheim Tel: 47-7288-4388

Poland - Warsaw Tel: 48-22-3325737

Romania - Bucharest Tel: 40-21-407-87-50

Spain - Madrid Tel: 34-91-708-08-90 Fax: 34-91-708-08-91

Sweden - Gothenberg Tel: 46-31-704-60-40 Sweden - Stockholm

Tel: 46-8-5090-4654

**UK - Wokingham** Tel: 44-118-921-5800 Fax: 44-118-921-5820