



MICROCHIP

**DAC-Based 4-20 mA
Current Loop
Reference Design**

Note the following details of the code protection feature on Microchip products:

- Microchip products meet the specifications contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is secure when used in the intended manner, within operating specifications, and under normal conditions.
- Microchip values and aggressively protects its intellectual property rights. Attempts to breach the code protection features of Microchip product is strictly prohibited and may violate the Digital Millennium Copyright Act.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of its code. Code protection does not mean that we are guaranteeing the product is "unbreakable" Code protection is constantly evolving. Microchip is committed to continuously improving the code protection features of our products.

This publication and the information herein may be used only with Microchip products, including to design, test, and integrate Microchip products with your application. Use of this information in any other manner violates these terms. Information regarding device applications is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. Contact your local Microchip sales office for additional support or, obtain additional support at <https://www.microchip.com/en-us/support/design-help/client-support-services>.

THIS INFORMATION IS PROVIDED BY MICROCHIP "AS IS". MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION INCLUDING BUT NOT LIMITED TO ANY IMPLIED WARRANTIES OF NON-INFRINGEMENT, MERCHANTABILITY, AND FITNESS FOR A PARTICULAR PURPOSE, OR WARRANTIES RELATED TO ITS CONDITION, QUALITY, OR PERFORMANCE.

IN NO EVENT WILL MICROCHIP BE LIABLE FOR ANY INDIRECT, SPECIAL, PUNITIVE, INCIDENTAL, OR CONSEQUENTIAL LOSS, DAMAGE, COST, OR EXPENSE OF ANY KIND WHATSOEVER RELATED TO THE INFORMATION OR ITS USE, HOWEVER CAUSED, EVEN IF MICROCHIP HAS BEEN ADVISED OF THE POSSIBILITY OR THE DAMAGES ARE FORESEEABLE. TO THE FULLEST EXTENT ALLOWED BY LAW, MICROCHIP'S TOTAL LIABILITY ON ALL CLAIMS IN ANY WAY RELATED TO THE INFORMATION OR ITS USE WILL NOT EXCEED THE AMOUNT OF FEES, IF ANY, THAT YOU HAVE PAID DIRECTLY TO MICROCHIP FOR THE INFORMATION.

Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights unless otherwise stated.

For information regarding Microchip's Quality Management Systems, please visit www.microchip.com/quality.

Trademarks

The Microchip name and logo, the Microchip logo, Adaptec, AVR, AVR logo, AVR Freaks, BesTime, BitCloud, CryptoMemory, CryptoRF, dsPIC, flexPWR, HELDO, IGLOO, JukeBlox, KeeLoq, Klear, LANCheck, LinkMD, maXStylus, maXTouch, MediaLB, megaAVR, Microsemi, Microsemi logo, MOST, MOST logo, MPLAB, OptoLyzer, PIC, picoPower, PICSTART, PIC32 logo, PolarFire, Prochip Designer, QTouch, SAM-BA, SenGenuity, SpyNIC, SST, SST Logo, SuperFlash, Symmetricom, SyncServer, Tachyon, TimeSource, tinyAVR, UNI/O, Vectron, and XMEGA are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

AgileSwitch, ClockWorks, The Embedded Control Solutions Company, EtherSynch, Flashtec, Hyper Speed Control, HyperLight Load, Libero, motorBench, mTouch, Powermite 3, Precision Edge, ProASIC, ProASIC Plus, ProASIC Plus logo, Quiet-Wire, SmartFusion, SyncWorld, TimeCesium, TimeHub, TimePictra, TimeProvider, and ZL are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Adjacent Key Suppression, AKS, Analog-for-the-Digital Age, Any Capacitor, AnyIn, AnyOut, Augmented Switching, BlueSky, BodyCom, Clockstudio, CodeGuard, CryptoAuthentication, CryptoAutomotive, CryptoCompanion, CryptoController, dsPICDEM, dsPICDEM.net, Dynamic Average Matching, DAM, ECAN, Espresso T1S, EtherGREEN, EyeOpen, GridTime, IdealBridge, IGaT, In-Circuit Serial Programming, ICSP, INICnet, Intelligent Paralleling, IntelliMOS, Inter-Chip Connectivity, JitterBlocker, Knob-on-Display, MarginLink, maxCrypto, maxView, memBrain, Minda, MiWi, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, mSiC, MultiTRAK, NetDetach, Omniscient Code Generation, PICDEM, PICDEM.net, PICKIT, PICtail, Power MOS IV, Power MOS 7, PowerSmart, PureSilicon, QMatrix, REAL ICE, Ripple Blocker, RTAX, RTG4, SAM-ICE, Serial Quad I/O, simpleMAP, SimpliPHY, SmartBuffer, SmartHLS, SMART-I.S., storClad, SQL, SuperSwitcher, SuperSwitcher II, Switchtec, SynchroPHY, Total Endurance, Trusted Time, TSHARC, Turing, USBCheck, VariSense, VectorBlox, VeriPHY, ViewSpan, WiperLock, XpressConnect, and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

The Adaptec logo, Frequency on Demand, Silicon Storage Technology, and Symmcom are registered trademarks of Microchip Technology Inc. in other countries.

GestIC is a registered trademark of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies.

© 2023, Microchip Technology Incorporated and its subsidiaries.

All Rights Reserved.

ISBN: 978-1-6683-3674-8

Table of Contents

Chapter 1. Reference Design Overview	
1.1 Introduction	9
1.1.1 4-20 mA Current Loop Overview	9
1.1.2 Feature Summary	11
1.1.3 Design Specifications	11
Chapter 2. Circuit Operation	
2.1 Circuit Description	13
2.2 Design Notes	14
2.3 Theory of Operation	14
Chapter 3. Tests and Results	
3.1 Simulation	19
3.2 Linearity Test	20
3.3 Current Output Drift	24
3.4 Temperature Drift	24
Appendix A. Schematic and Layouts	
A.1 Introduction	25
A.2 Board – Schematic	26
A.3 Board – Top Assembly	27
A.4 Board – Bottom Assembly	27
A.5 Board – Top View	28
A.6 Board – Bottom View	28
Appendix B. Bill of Materials (BOM)	29

DAC-Based 4-20 mA Current Loop Reference Design

NOTES:

Preface

NOTICE TO CUSTOMERS

All documentation becomes dated, and this manual is no exception. Microchip tools and documentation are constantly evolving to meet customer needs, so some actual dialogs and/or tool descriptions may differ from those in this document. Please refer to our website (www.microchip.com) to obtain the latest documentation available.

Documents are identified with a “DS” number. This number is located on the bottom of each page, in front of the page number. The numbering convention for the DS number is “DSXXXXXXXXA”, where “XXXXXXXX” is the document number and “A” is the revision level of the document.

For the most up-to-date information on development tools, see the MPLAB® IDE online help. Select the Help menu, and then Topics to open a list of available online help files.

INTRODUCTION

This chapter contains general information that will be useful to know before using the DAC-Based 4-20 mA Current Loop. Items discussed in this chapter include:

- [Document Layout](#)
- [Conventions Used in this Guide](#)
- [Recommended Reading](#)
- [The Microchip Website](#)
- [Customer Support](#)
- [Document Revision History](#)

DOCUMENT LAYOUT

This document describes how to design the DAC-Based 4-20 mA Current Loop transmitter with MCP48CMD2X DAC family. The manual layout is as follows:

- **Chapter 1. “Reference Design Overview”** – Provides the insight on 4-20mA current loop industry standard.
- **Chapter 2. “Circuit Operation”** – Provides the DAC-Based 4-20 mA transmitter circuit operation.
- **Chapter 3. “Tests and Results”** – Shows the result of performed tests on EV34C35A DAC-Based 4-20 mA Current Loop transmitter board.
- **Appendix A. “Schematic and Layouts”** – Shows the schematic and layout diagrams for the EV34C45A DAC-Based 4-20 mA Current Loop.
- **Appendix B. “Bill of Materials (BOM)”** – Lists the parts used to build the EV34C45A DAC-Based 4-20 mA Current Loop transmitter board.

DAC-Based 4-20 mA Current Loop Reference Design

CONVENTIONS USED IN THIS GUIDE

This manual uses the following documentation conventions:

DOCUMENTATION CONVENTIONS

Description	Represents	Examples
Arial font:		
Italic characters	Referenced books	<i>MPLAB® IDE User's Guide</i>
	Emphasized text	...is the <i>only</i> compiler...
Initial caps	A window	the Output window
	A dialog	the Settings dialog
	A menu selection	select Enable Programmer
Quotes	A field name in a window or dialog	"Save project before build"
Underlined, Italic text with right angle bracket	A menu path	<u>File</u> > <i>Save</i>
Bold characters	A dialog button	Click OK
	A tab	Click the Power tab
N'Rnnnn	A number in verilog format, where N is the total number of digits, R is the radix and n is a digit.	4'b0010, 2'hF1
Text in angle brackets < >	A key on the keyboard	Press <Enter>, <F1>
Courier New font:		
Plain Courier New	Sample source code	#define START
	Filenames	autoexec.bat
	File paths	c:\mcc18\h
	Keywords	_asm, _endasm, static
	Command-line options	-Opa+, -Opa-
	Bit values	0, 1
	Constants	0xFF, 'A'
Italic Courier New	A variable argument	<i>file.o</i> , where <i>file</i> can be any valid filename
Square brackets []	Optional arguments	mcc18 [options] <i>file</i> [options]
Curly brackets and pipe character: { }	Choice of mutually exclusive arguments; an OR selection	errorlevel {0 1}
Ellipses...	Replaces repeated text	var_name [, var_name...]
	Represents code supplied by user	void main (void) { ... }

RECOMMENDED READING

This reference design provides the design overview, theory of operation and test results of the DAC-Based 4-20 mA Current Loop transmitter. Another useful document is listed below. The following Microchip documents are available and recommended as a supplemental reference resource.

- **EV34C35A DAC Based 4-20 mA Current Loop Evaluation Board User's Guide (DS50003613)**

THE MICROCHIP WEBSITE

Microchip provides online support via our website at www.microchip.com. This website is used as a means to make files and information easily available to customers. Accessible by using your favorite Internet browser, the website contains the following information:

- **Product Support** – Data sheets and errata, application notes and sample programs, design resources, user's guides and hardware support documents, latest software releases and archived software
- **General Technical Support** – Frequently Asked Questions (FAQs), technical support requests, online discussion groups, Microchip consultant program member listing
- **Business of Microchip** – Product selector and ordering guides, latest Microchip press releases, listing of seminars and events, listings of Microchip sales offices, distributors and factory representatives

CUSTOMER SUPPORT

Users of Microchip products can receive assistance through several channels:

- Distributor or Representative
- Local Sales Office
- Embedded System Engineer (ESE)
- Technical Support

Customers should contact their distributor, representative or field application engineer (FAE) for support. Local sales offices are also available to help customers. A listing of sales offices and locations is included in the back of this document.

Technical support is available through the website at:

<http://www.microchip.com/support>.

DAC-Based 4-20 mA Current Loop Reference Design

DOCUMENT REVISION HISTORY

Revision A (December 2023)

- Initial release of this document.

Chapter 1. Reference Design Overview

1.1 INTRODUCTION

This chapter provides an overview of the DAC-Based 4-20 mA Current Loop Reference Design and covers the following topics:

- [4-20 mA Current Loop Overview](#)
- [Feature Summary](#)
- [Design Specifications](#)

1.1.1 4-20 mA Current Loop Overview

In the 1950-1960 era, mechanical dominant process control industry transitioned from pneumatic control to electrical signal control. Analog signals became the medium where the information about the different process variables is transmitted via voltage or current. In the world of wireless and wired transmission systems, 4-20 mA current loop is a dominant industry standard. High accuracy, low complexity with cost effectiveness of the 4-20 mA current loop stands out against the other transmission methods. MCP48CMD21 DAC-Based 4-20 mA Current Loop transmitter offers a reliable solution with high accuracy.

There are different systems in place to use 4-20 mA current loop for processing variables and transmit control signals. [Figure 1-1](#), [Figure 1-2](#) and [Figure 1-3](#) show a 2-wire, 3-wire and 4-wire system block diagram.

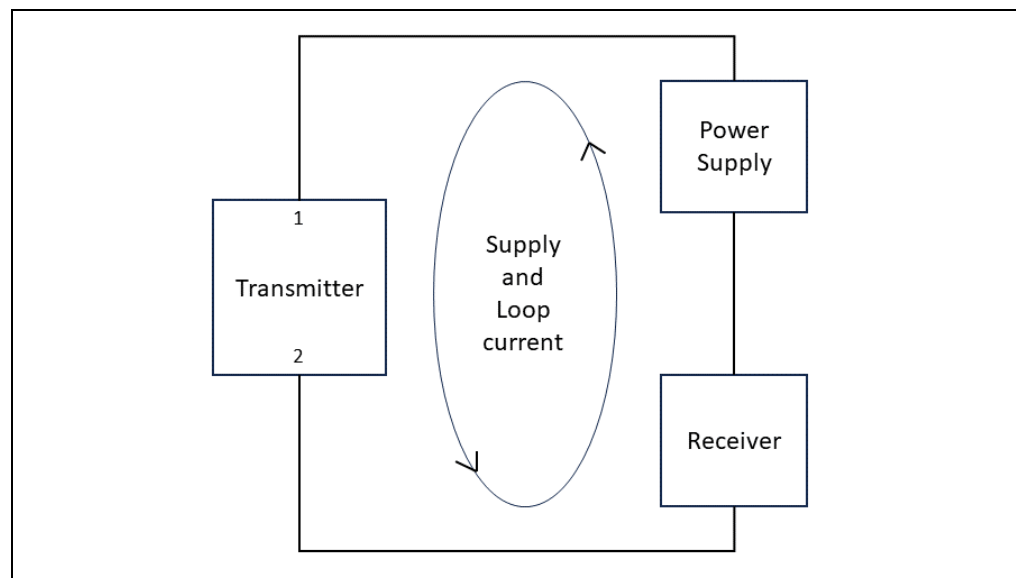


FIGURE 1-1: 2-Wire Connection.

DAC-Based 4-20 mA Current Loop Reference Design

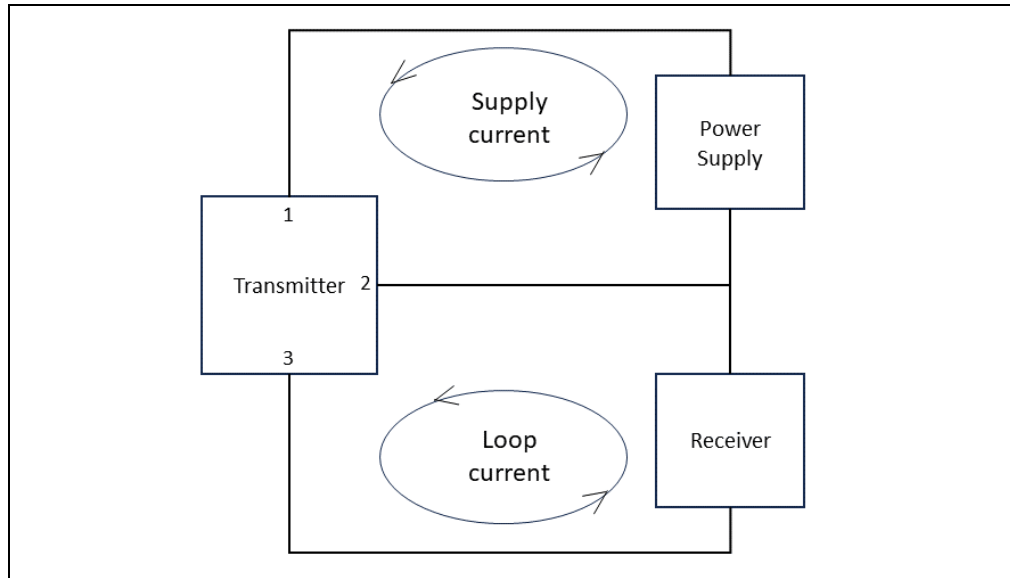


FIGURE 1-2: 3-Wire Connections.

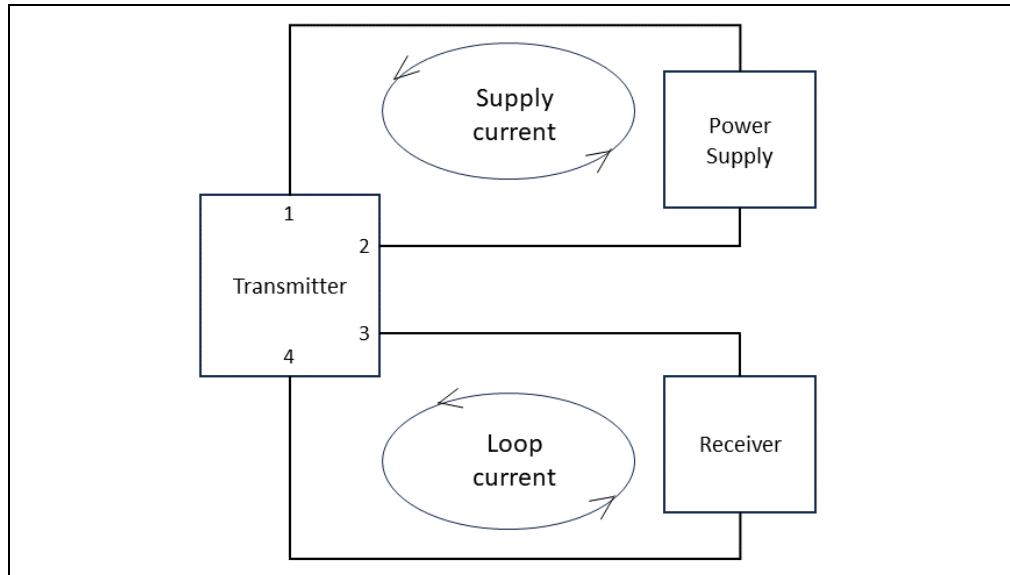


FIGURE 1-3: 4-Wire Connections.

Microchip's DAC-Based 4-20 mA Current Loop reference design is based on the 2-wire connection systems. Following are the main components in the 2-wire current loop system:

- Sensor
- Transmitter
- Receiver
- System Power Supply
- Loop wire

Microchip's DAC-Based 4-20 mA Current Loop reference design is about the transmitter which converts process signal into 4-20 mA current and transmits it over a long distance.

1.1.2 Feature Summary

- High Accuracy
- Current budgeting with room to allocate different system level alarms
- Offset adjustment at 4 mA
- Small size printed circuit board (PCB)
- Low-cost design

1.1.3 Design Specifications

	Parameter		Specifications
Input	DAC Voltage	V_{DAC_min}	0V
		V_{DAC_max}	2.5V
Output	Loop current	I_{loop_min}	4 mA
		I_{loop_max}	20 mA
Supply	Loop Power Supply	V_{Loop}	24V
Load	Resistive load	R_{Load}	250 Ω

DAC-Based 4-20 mA Current Loop Reference Design

NOTES:

Chapter 2. Circuit Operation

2.1 CIRCUIT DESCRIPTION

DAC Based 4-20 mA Current Loop reference design of transmitter is designed to regulate the loop current according to the changes in the process variable value. Sensor output computed by the host controller (MCU) is provided through MCP48CMD21, a 12-bit 1LSb DAC as an input to current loop transmitter. MCP4152 is an 8-bit digipot that provides an offset trimming option at the lower end of current. MCP1501 is an external voltage reference that provides the precise output to DAC reference and helps to improve accuracy. Loop current flows through the return wire in 2-wire systems, thus it is necessary that the quiescent current of the transmitter and other devices in the loop is less than the minimum loop current. Appropriate current budgeting allows users to allocate alarms for system failures.

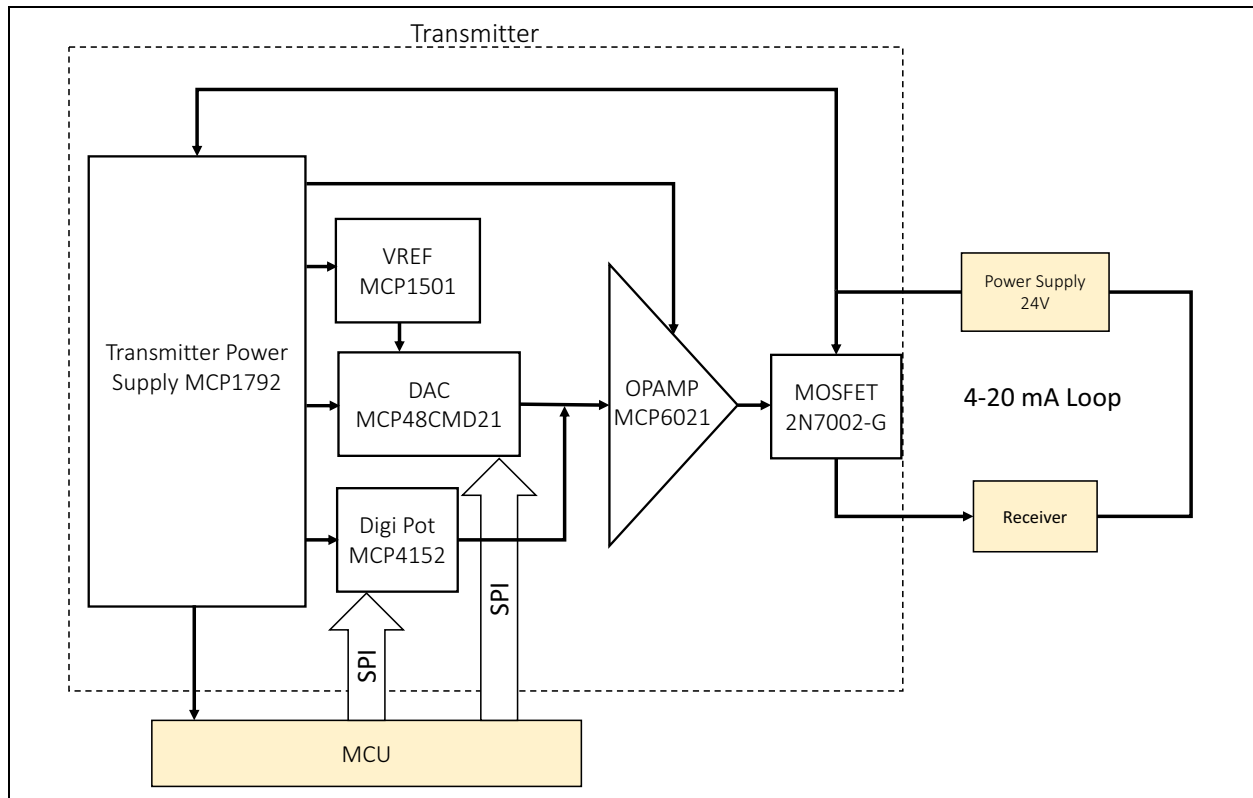


FIGURE 2-1: Block Diagram of 4-20 mA Current Reference Design.

DAC-Based 4-20 mA Current Loop Reference Design

2.2 DESIGN NOTES

1. For high accuracy, resistors with low tolerance (1%, 0.5% or 0.1%) are recommended.
2. Transmitter design has a floating ground for the current's return path, and it is different than the power supply ground.
3. Current budgeting with quiescent current from all the devices including MCU in the loop must be below 3.6 mA.
4. The current flowing through the MOSFET needs to be limited for proper operation.
5. Digipot selection depends on application requirement.

Note: Please refer to [Appendix A. "Schematic and Layouts"](#) for the schematic and [Table 2-1](#) for current budgeting, which lists out the quiescent current of the components used in the transmitter board. This total current includes the current for the MCU controlling the DAC and digipot.

2.3 THEORY OF OPERATION

DAC Based 4-20 mA Current Loop reference design accepts DAC voltage and converts it to a current in such a way that the relation between input process variable and the output loop current is linear. The design specification table provides the relationship between DAC voltage and the loop current. DAC Based 4-20 mA Current Loop reference design circuit diagram is shown in [Figure 2-2](#).

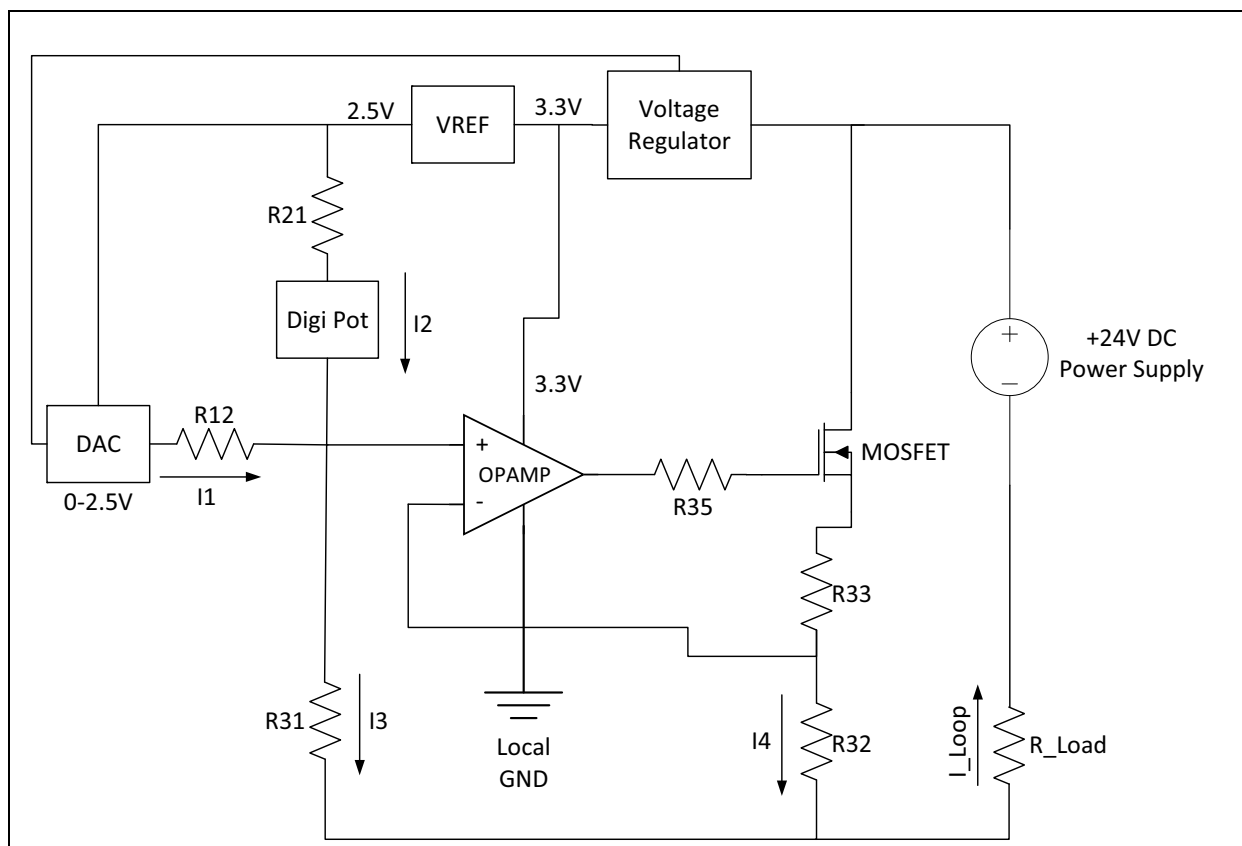


FIGURE 2-2: Circuit Diagram of 4-20 mA Current Loop Transmitter.

Installation and Operation

The loop current I_{Loop} is the sum of the currents flowing through R31 and R32, which are denoted by $I3$ and $I4$.

EQUATION 2-1:

$$I_{Loop} = I3 + I4$$

$I3$ is a combination of the current flowing from R12 and R21, assigned as $I1$ and $I2$.

EQUATION 2-2:

$$I3 = I1 + I2$$

In this design, op amp inverting terminal is connected to return path which can be called local ground for the future reference in this design. All the devices including voltage regulator, voltage reference, DAC, digipot and op amp return paths are connected to this local ground. An external MCU who computes the sensor output shares this local ground as well.

$I3$ can be calculated from [Equation 2-3](#).

EQUATION 2-3:

$$I3 = \frac{V_{DAC}}{R12} + \frac{V_{REF}}{R21}$$

Summation of all the local return currents and the current through MOSFET compensate the remaining loop current other than $I3$. The potential at the non-inverting input terminal will be driven to local ground due to negative feedback. The voltages across R31 and R32 must be equal for proper operation of the op amp. Assuming voltage across R31 is $V3$ and voltage across R32 is $V4$, where ($V3 = V4$) gives:

EQUATION 2-4:

$$I3 \times R31 = R32 \times I4$$

By rearranging [Equation 2-4](#):

EQUATION 2-5:

$$I4 = I3 \times \frac{R31}{R32}$$

[Equation 2-1](#) can be rewritten as shown in [Equation 2-6](#):

EQUATION 2-6:

$$I_{Loop} = I3 \left(1 + \frac{R31}{R32} \right)$$

This equation indicates the loop current dependency on $I3$ and provides the relationship between loop current and input.

Linear operation of circuit depends on [Equation 2-7](#):

EQUATION 2-7:

$$\frac{I3_{min}}{I3_{max}} = \frac{I_{Loop_{min}}}{I_{Loop_{max}}}$$

DAC-Based 4-20 mA Current Loop Reference Design

Design requirements are set with $I_{Loop_min} = 4 \text{ mA}$ and $I_{Loop_max} = 20 \text{ mA}$. Substitute these values in [Equation 2-7](#):

EQUATION 2-8:

$$\frac{I3_{min}}{I3_{max}} = \frac{4}{20} = \frac{1}{5}$$

As per circuit diagram and [Equation 2-2](#):

EQUATION 2-9:

$$I3 = \frac{V_{DAC}}{R12} + \frac{V_{REF}}{R21}$$

- $I1$ is the current flowing through $R12$ and depends on the V_{DAC} . It is a driving force for the loop current.
- $I2$ is the current from digipot which can be used for calibration. Ideally, $I2 = I3$ when V_{DAC} is not present. As per [Equation 2-6](#), $I3$ is directly proportional to I_{Loop} . So, for this design, $I2$ is assumed at $40 \mu\text{A}$.

From [Equation 2-2](#), it can be concluded that $I3_{min} = 40 \mu\text{A}$ when $I1 = 0$. Then, $I3_{max} = 40 \mu\text{A} \times 5 = 200 \mu\text{A}$ as per [Equation 2-8](#).

$$I3_{min} = \frac{V_{DAC_{min}}}{R12} + \frac{V_{REF}}{R21}$$

$$40 \mu\text{A} = \frac{0}{R12} + \frac{2.5\text{V}}{R21}$$

$$R21 = \frac{2.5\text{V}}{40 \mu\text{A}} = 62.5\text{K}$$

For offset trimming, $R21 = 47\text{K}$ in series with digipot is selected. Digipot will provide an option to trim the lower value exactly at 4 mA .

For $V_{DAC} = 2.5\text{V}$, [Equation 2-10](#) will be as follows:

EQUATION 2-10:

$$I3_{max} = \frac{V_{DAC_{max}}}{R12} + \frac{V_{REF}}{R21}$$

$$200 \mu\text{A} = \frac{2.5\text{V}}{R12} + \frac{2.5\text{V}}{62.5\text{K}}$$

$$R1 = \frac{2.5\text{V}}{160 \mu\text{A}} = 15.6\text{K}$$

In design, 15K is selected for the $R12$ and the digipot is given headroom to trim the 4 mA current.

As per [Equation 2-6](#), gain of the current loop is set by $R31$ and $R32$.

EQUATION 2-11:

$$I_{Loop_min} = I3_min \left(1 + \frac{R31}{R32} \right)$$

$$4 \text{ mA} = 40 \mu\text{A} \left(1 + \frac{R31}{R32} \right)$$

EQUATION 2-12:

$$\frac{R31}{R32} = 99$$

R31 = 2.2K and R32 = 22Ω are selected respectively in this design. Selecting R32 in this design is important as the higher value of R32 may exhibit headroom issues for regulator input voltage. The load voltage at maximum load current is:

- V_Load = I_Loop_max x R_Load
- V_Load = 20 mA x 250Ω
- V_Load = 5V

Most of the loop current comes through MOSFET and flows through R32 and R33. Assume 20 mA flows through R32. Voltage at local ground node is calculated by the following relation:

- V_local_gnd = V_Load + R32 x 20 mA

To provide the enough headroom, R32 = 22Ω is selected.

- V_local_gnd = 5V + 0.4V = 5.4V

Headroom voltage = 24 - 5.4V = 18.6V

This will provide more than enough head room for LDO input and prevent it from entering dropout and affecting the linear performance of current loop.

Current budgeting for the board is essential for 4-20 mA current loop system performance.

[Table 2-1](#) shows the current budgeting for DAC Based 4-20 mA Current Loop board design.

TABLE 2-1:

Device	Part Number	Supply Current
Regulator	MCP1792 (3.3V)	45 μA
DAC	MCP48CMD21	140 μA
VREF	MCP1501 (2.5V)	350 μA
Digipot	MCP4152	5 μA
Op Amp	MCP6021	1.3 mA
MOSFET	2N7002	1 μA
Total Transmitter Current =		1.8 mA approximately

The microcontroller (MCU) can be selected as per permitted loop current. For example, if 4-20 mA current loop system is set for 3.6 mA fault alarm, total current consumption for the transmitter board and MCU have to be less than 3.6 mA.

Therefore, MCU current has to be limited around 1.8 mA as per total current required at transmitter (see [Table 2-1](#)).

DAC-Based 4-20 mA Current Loop Reference Design

NOTES:

Chapter 3. Tests and Results

3.1 SIMULATION

DAC Based 4-20 mA Current Loop circuit is simulated with dummy DAC supply in MPLAB MINDI software. DAC voltage is swept from 0V to 2.5V and output current is observed from 4 mA to 20 mA.

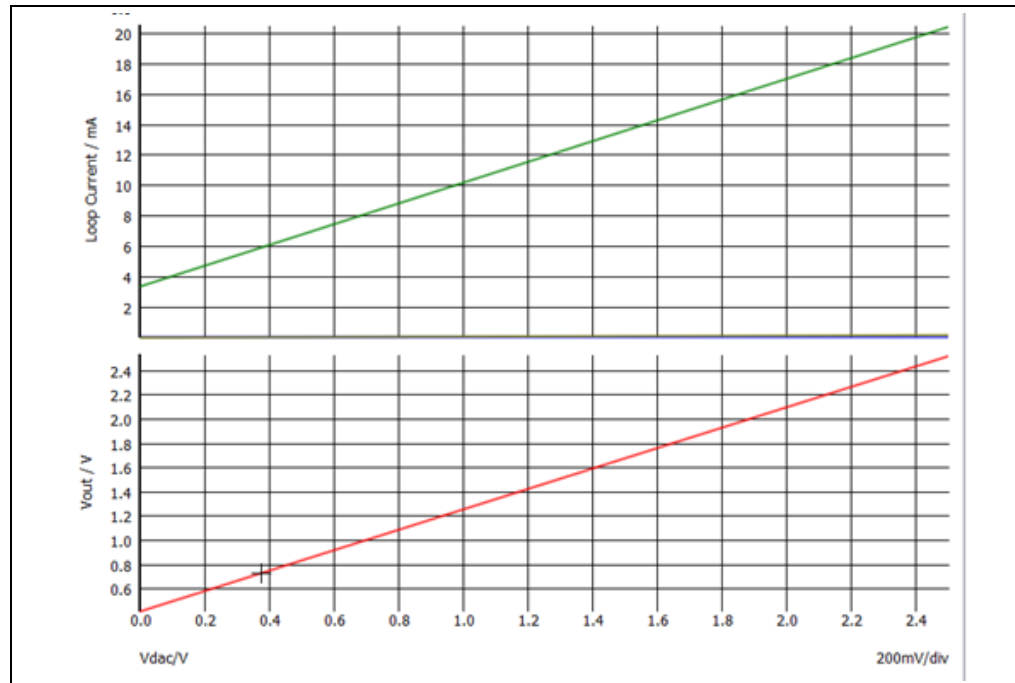


FIGURE 3-1: *Simulation Result.*

DAC-Based 4-20 mA Current Loop Reference Design

3.2 LINEARITY TEST

As shown in [Section 2.3 “Theory of Operation”](#), the output current depends on the DAC voltage. Accuracy and linearity mainly depend on the DAC performance.

[Figure 3-2](#) shows the block diagram of the DAC system and [Figure 3-3](#) shows the 12-bit DAC performance when code swept from 0 to 4095.

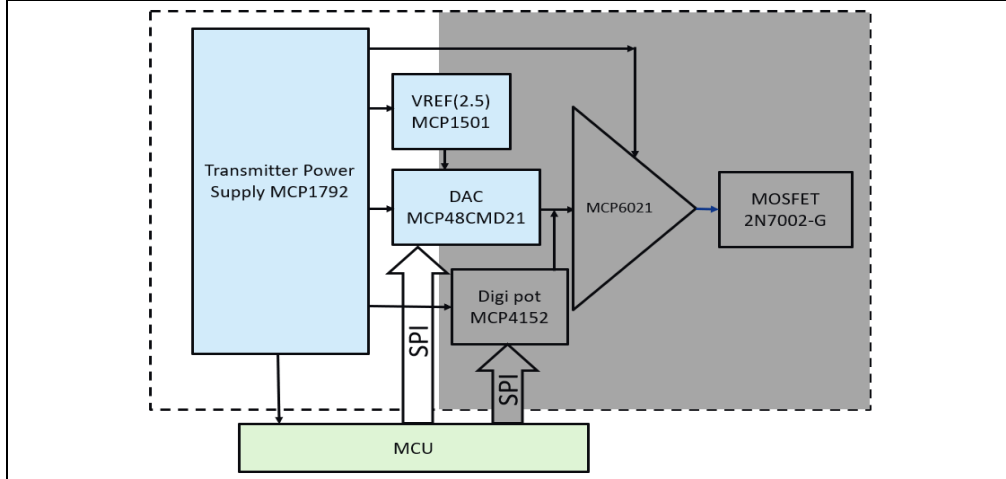


FIGURE 3-2: DAC Subsystem Block Diagram.

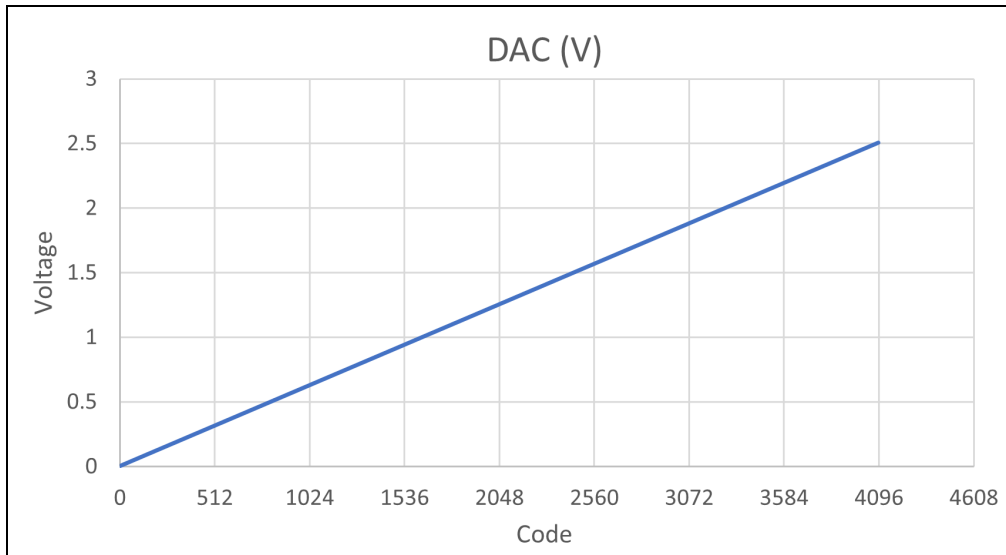


FIGURE 3-3: DAC Subsystem Output Voltage.

DAC subsystem DNL and INL performance are shown in [Figure 3-4](#) and [Figure 3-5](#).

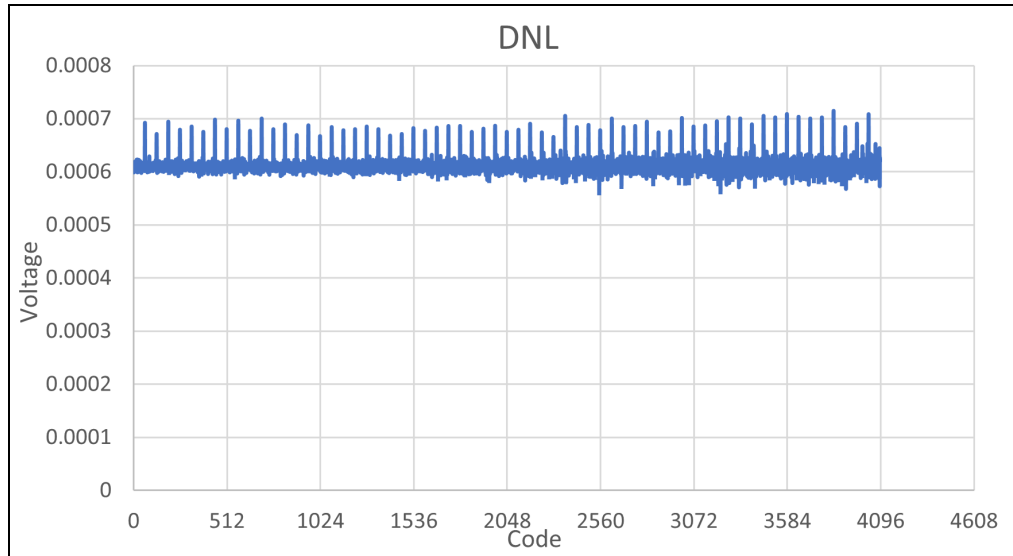


FIGURE 3-4: DAC Subsystem DNL.

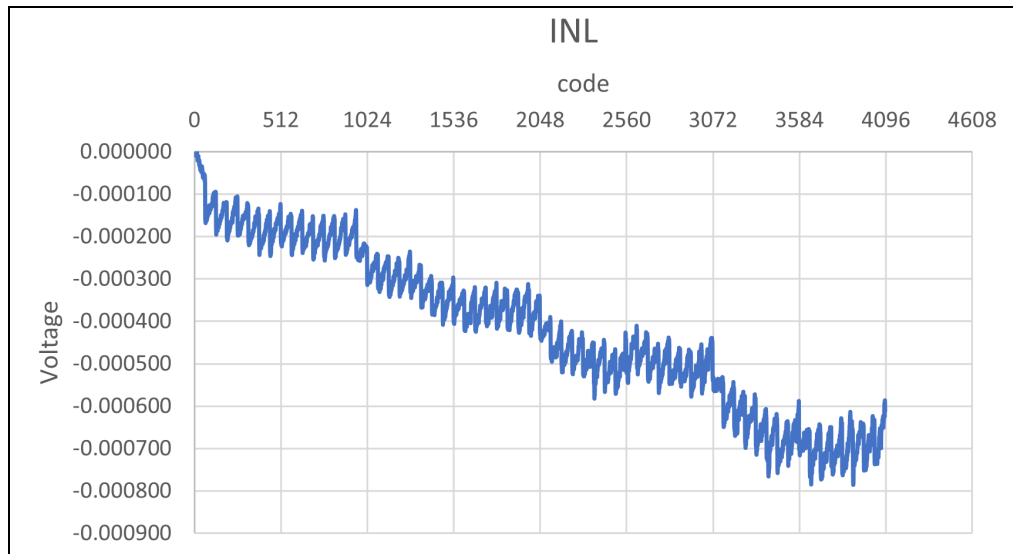


FIGURE 3-5: DAC Subsystem INL.

Looking at the differential nonlinearity, each code is 1 LSb apart from each other for the entire DAC code range and the INL graph also shows around 1 LSb error over entire code range.

[Figure 2-1](#) shows the complete 4-20 mA current loop transmitter block diagram.

Performance of the 4-20 mA current loop system over the 0 to 4095 DAC code range is shown in [Figure 3-6](#), [Figure 3-7](#) and [Figure 3-8](#).

DAC-Based 4-20 mA Current Loop Reference Design

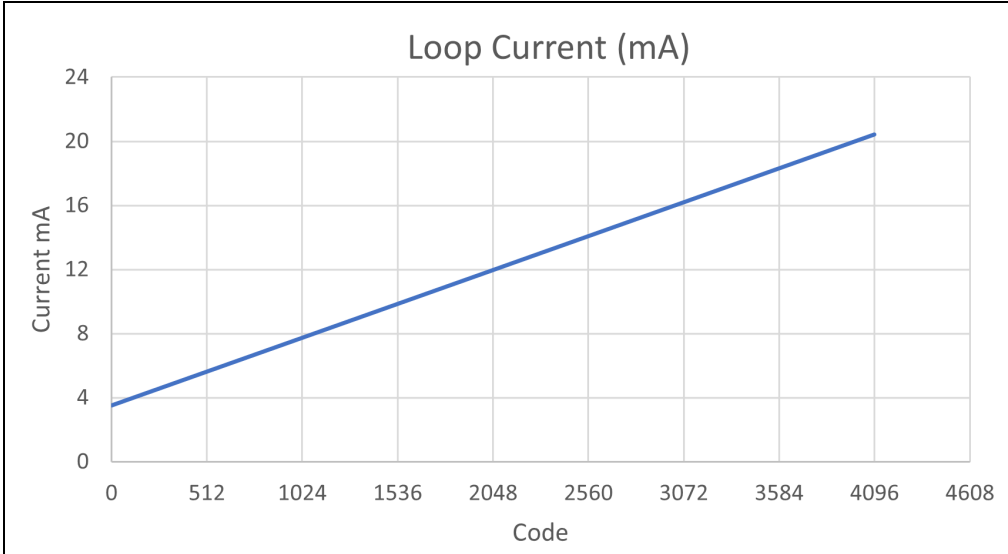


FIGURE 3-6: Transmitter Loop Current.

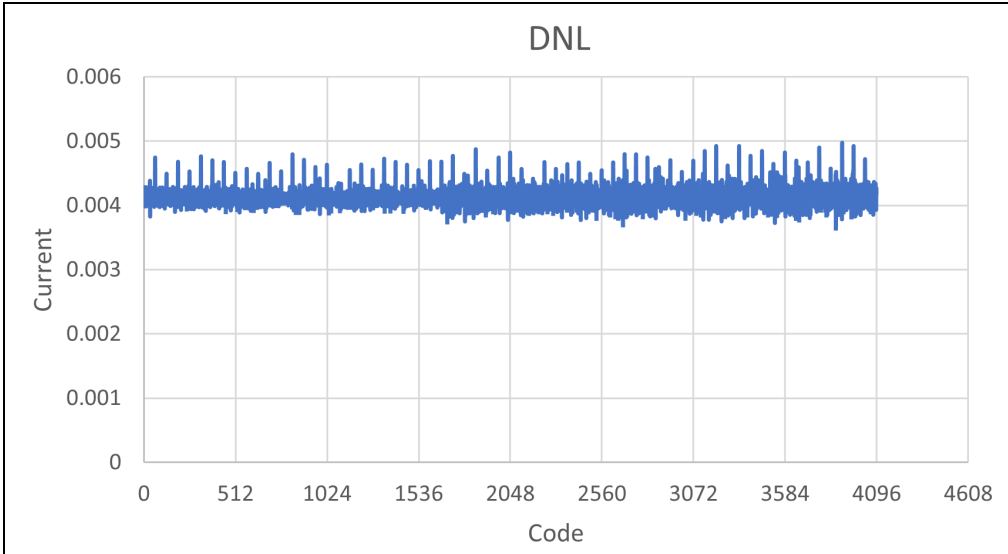


FIGURE 3-7: Transmitter Loop Current DNL.

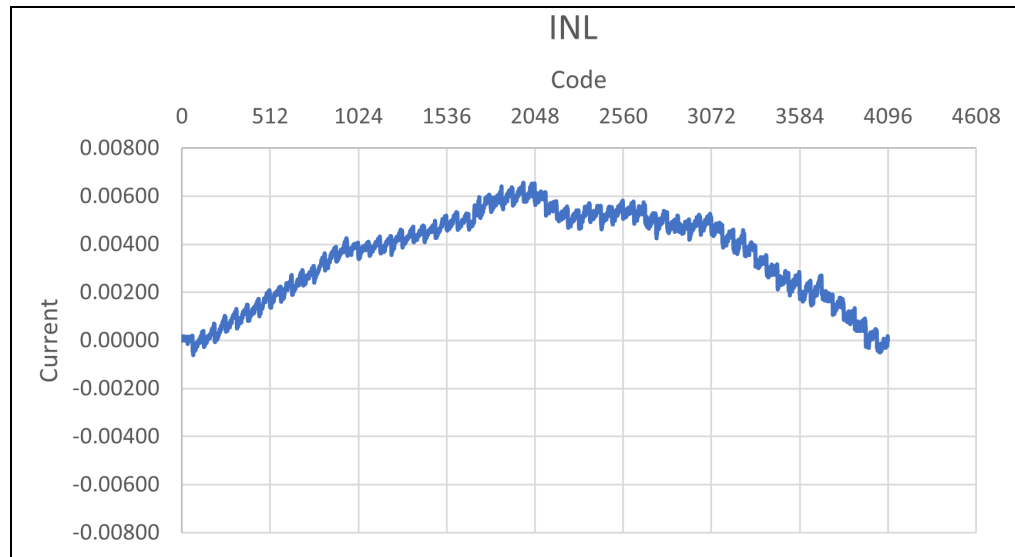


FIGURE 3-8: *Transmitter Loop Current INL.*

From the graphs, it is visible that the relation between DAC voltage and loop current is linear over the entire 0 to 4095 code range. INL and DNL graphs show the complete system error is within 1 LSB.

DAC-Based 4-20 mA Current Loop Reference Design

3.3 CURRENT OUTPUT DRIFT

This test was conducted under a room temperature (not in a controlled temperature environment or heat chamber) on a work bench set up. The test run time was 48 hours. Result shows the amount of change of a measured current reading at ambient conditions over a given period.

The following tables show the test results for output drift at 4 mA and 20 mA.

Output Drift	
Minimum	4.000554 mA
Maximum	4.001863 mA
Average	4.001125 mA
Total Count (Readings)	734381

Output Drift	
Minimum	19.99856 mA
Maximum	20.00164 mA
Average	19.99985 mA
Total Count (Readings)	738152

- % Drift Error over 4-20 mA span is calculated by the following formula:
- % Drift = (Maximum current reading - minimum current reading)/16 mA x 100

The drift error at ambient temperature is around 0.01% - 0.02% of the span.

3.4 TEMPERATURE DRIFT

Output drift test over the temperature range from (-25°C to +60°C) is performed using temperature oven. Output drift of 5 boards is observed at -25°C, 0°C, +25°C and +60°C temperature points. The temperature of the oven is set at each set point for 2 hours and collects the output data. The graph in [Figure 3-9](#) shows the average of the temp drift at each temperature set point. It is observed the % temperature drift error is below 0.02%.

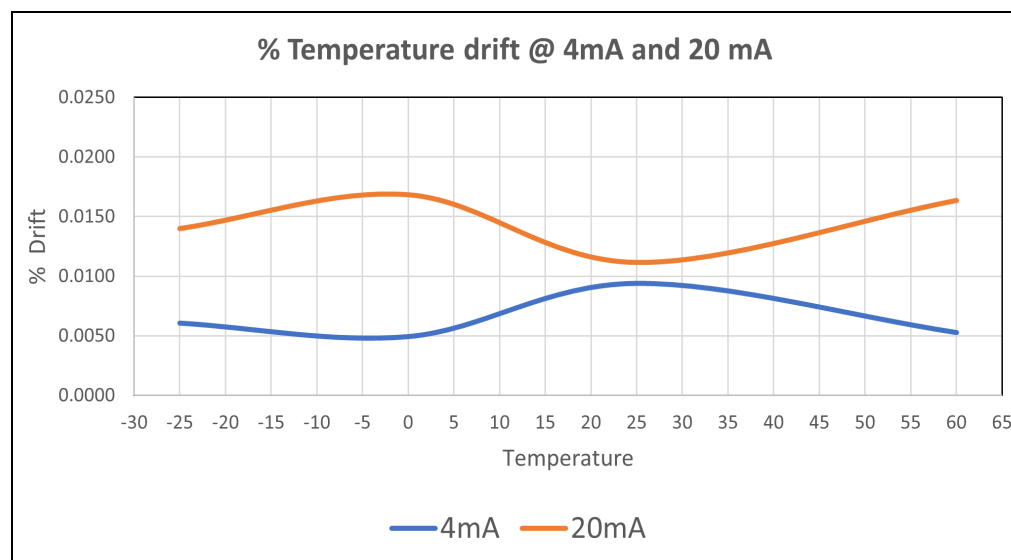


FIGURE 3-9: Temperature Drift.

Appendix A. Schematic and Layouts


A.1 INTRODUCTION

This appendix contains the following schematics and layouts for the DAC Based 4-20 mA Current Loop:


- [Board – Schematic](#)
- [Board – Top Assembly](#)
- [Board – Bottom Assembly](#)
- [Board – Top View](#)
- [Board – Bottom View](#)

A.2 BOARD – SCHEMATIC


LDO: 3.3V, 100mA (3 lead SOT-23A)

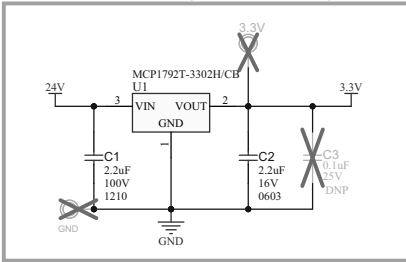

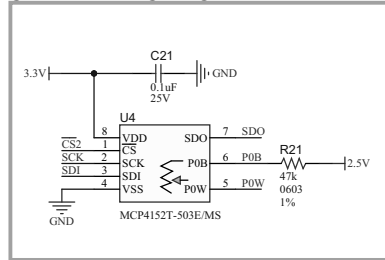
Digi Pot: 8-Bit Single Digital POT with NVM and SPI (DFN-8)




MCU Connector

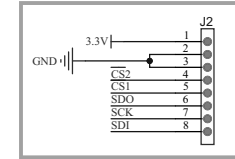

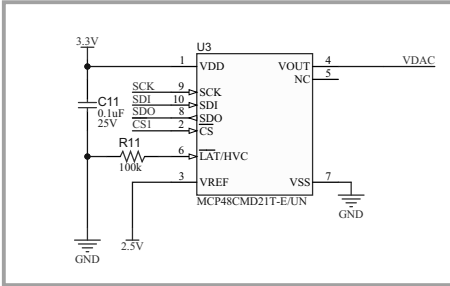
DAC: 12-bit, Single channel, SPI (MSOP-10)



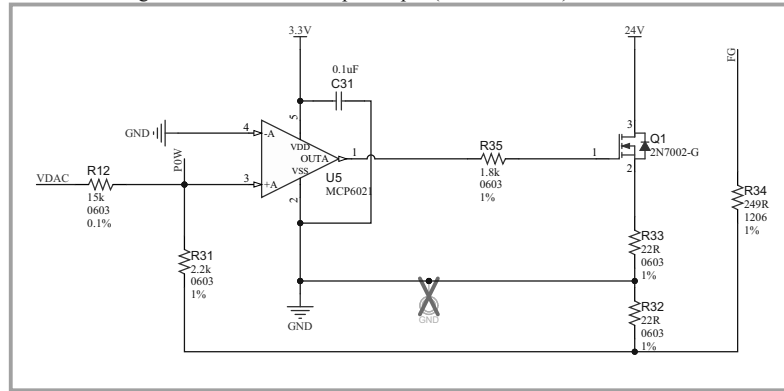
OPAMP: Single channel rail to rail input/output (5 lead SOT-23)




24V Supply

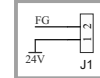


VREF: 2.5V, 50ppm (6 lead SOT-23)

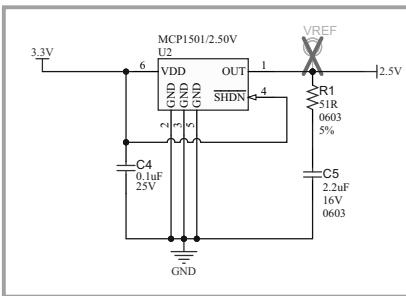

A.3 BOARD – TOP ASSEMBLY

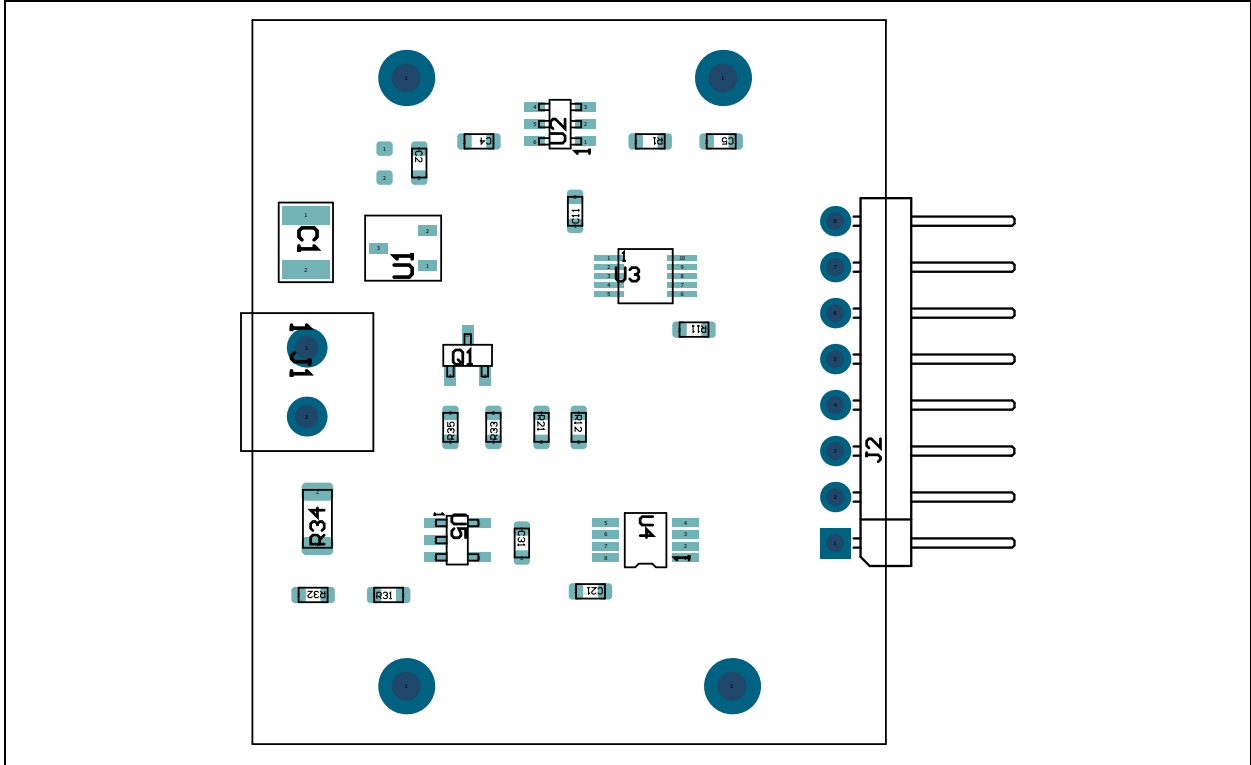

A.4 BOARD – BOTTOM ASSEMBLY

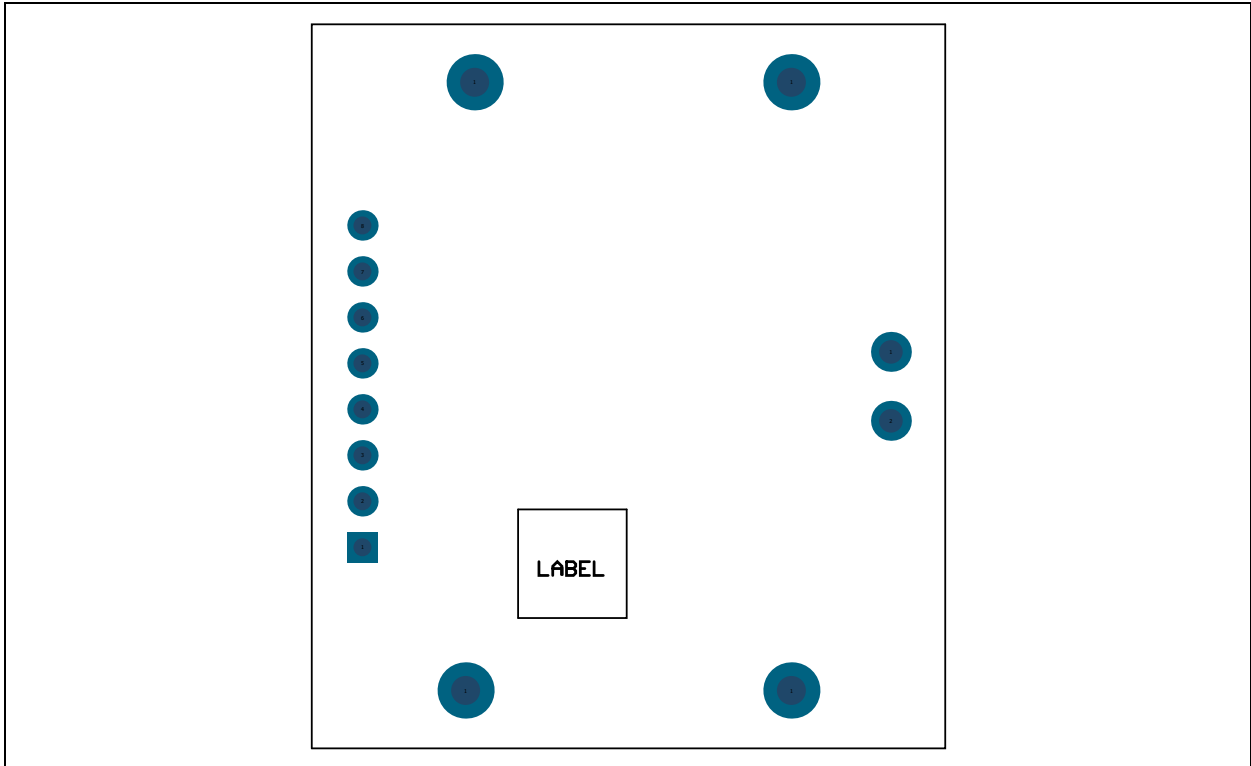

Appendix B. Bill of Materials (BOM)

TABLE B-1: BILL OF MATERIALS (BOM)

Qty.	Reference	Description	Manufacturer	Part Number
1	C1	CAP CER 2.2 μ F 100V 10% X7R SMD 1210	Samsung Electro-Mechanics America, Inc.	CL32B225KCJSNNE
2	C2, C5	CAP CER 2.2 μ F 16V 10% X5R SMD 0603	TDK Corporation	C1608X5R1C225K080AB
0	C3	CAP CER 0.1 μ F 25V 10% X7R SMD 0603 – Do Not Populate	KEMET	C0603C104K3RAC7013
4	C4, C11, C21, C31	CAP CER 0.1 μ F 25V 10% X7R SMD 0603	KEMET	C0603C104K3RAC7013
1	J1	CON TERMINAL 3.81 mm 1x2 Female 16-30AWG 13.5A TH R/A	Phoenix Contact	1727010
1	J2	CON HDR-2.54 Male 1x8 Gold 5.84MH TH R/A	Sullins Connector Solutions	PBC08SBAN
1	LABEL	LABEL PCBA 6x6 mm Info Text	ACT Logimark AS	505462
1	PCB1	Printed Circuit Board – DAC Based 4-20 mA Current Loop	Microchip Technology Inc.	04-11954-R1
1	Q1	MCHP ANALOG MOSFET N-CH 2N7002-G 60V 115 mA SOT-23-3	Microchip Technology Inc.	2N7002-G
1	R1	RES TKF 51R 5% 1/10W SMD 0603	Panasonic® – ECG	ERJ-3GEYJ510V
1	R11	RES TKF 100 k Ω 5% 1/10W SMD 0603 AEC-Q200	Panasonic – ECG	ERJ-3GEYJ104V
1	R12	RES TF 15 k Ω 0.1% 1/10W SMD 0603	Panasonic – ECG	ERA-3AEB153V
1	R21	RES TKF 47 k Ω 1% 1/10W SMD 0603	Panasonic – ECG	ERJ-3EKF4702V
1	R31	RES TKF 2.2 k Ω 1% 1/10W SMD 0603	Panasonic – ECG	ERJ-3EKF2201V
2	R32, R33	RES TKF 22R 1% 1/10W SMD 0603	Panasonic – ECG	ERJ-3EKF22R0V
1	R34	RES TKF 249R 1% 1/4W SMD 1206	ROHM Semiconductor	MCR18EZH2490
1	R35	RES TKF 1.8 k Ω 1% 1/10W SMD 0603	Panasonic – ECG	ERJ-3EKF1801V
0	3.3V, TP1, TP2, VREF	CON TP LOOP Red TH – Do Not Populate	Keystone® Electronics Corp.	5010
1	U1	MCHP ANALOG VOLTAGE REGULATOR 3.3V 3LD MCP1792T-3302H/CB SOT-23A-3	Microchip Technology Inc.	MCP1792T-3302H/CB
1	U2	MCHP ANALOG VREF 2.50V MCP1501T-25E/CHY SOT-23-6	Microchip Technology Inc.	MCP1501T-25E/CHY

DAC-Based 4-20 mA Current Loop Reference Design

TABLE B-1: BILL OF MATERIALS (BOM) (CONTINUED)

Qty.	Reference	Description	Manufacturer	Part Number
1	U3	MCHP ANALOG DAC 1-Ch 12-bit MCP48CMD21T-E/UN MSOP-10	Microchip Technology Inc.	MCP48CMD21T-E/UN
1	U4	MCHP ANALOG DIGIPOT 50KOHM 257TAP 8MSOP	Microchip Technology Inc.	MCP4152T-503E/MS
1	U5	MCHP ANALOG OPAMP 1-Ch 10MHz MCP6021T-E/OT SOT-23-5	Microchip Technology Inc.	MCP6021T-E/OT



MICROCHIP

Worldwide Sales and Service

AMERICAS

Corporate Office
2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support:
<http://www.microchip.com/support>
Web Address:
www.microchip.com

Atlanta

Duluth, GA
Tel: 678-957-9614
Fax: 678-957-1455

Austin, TX

Tel: 512-257-3370

Boston

Westborough, MA
Tel: 774-760-0087
Fax: 774-760-0088

Chicago

Itasca, IL
Tel: 630-285-0071
Fax: 630-285-0075

Dallas

Addison, TX
Tel: 972-818-7423
Fax: 972-818-2924

Detroit

Novi, MI
Tel: 248-848-4000

Houston, TX

Tel: 281-894-5983

Indianapolis

Noblesville, IN
Tel: 317-773-8323
Fax: 317-773-5453
Tel: 317-536-2380

Los Angeles

Mission Viejo, CA
Tel: 949-462-9523
Fax: 949-462-9608
Tel: 951-273-7800

Raleigh, NC

Tel: 919-844-7510

New York, NY

Tel: 631-435-6000

San Jose, CA

Tel: 408-735-9110
Tel: 408-436-4270

Canada - Toronto

Tel: 905-695-1980
Fax: 905-695-2078

ASIA/PACIFIC

Australia - Sydney
Tel: 61-2-9868-6733

China - Beijing
Tel: 86-10-8569-7000

China - Chengdu
Tel: 86-28-8665-5511

China - Chongqing
Tel: 86-23-8980-9588

China - Dongguan
Tel: 86-769-8702-9880

China - Guangzhou
Tel: 86-20-8755-8029

China - Hangzhou
Tel: 86-571-8792-8115

China - Hong Kong SAR
Tel: 852-2943-5100

China - Nanjing
Tel: 86-25-8473-2460

China - Qingdao
Tel: 86-532-8502-7355

China - Shanghai
Tel: 86-21-3326-8000

China - Shenyang
Tel: 86-24-2334-2829

China - Shenzhen
Tel: 86-755-8864-2200

China - Suzhou
Tel: 86-186-6233-1526

China - Wuhan
Tel: 86-27-5980-5300

China - Xian
Tel: 86-29-8833-7252

China - Xiamen
Tel: 86-592-2388138

China - Zhuhai
Tel: 86-756-3210040

ASIA/PACIFIC

India - Bangalore
Tel: 91-80-3090-4444

India - New Delhi
Tel: 91-11-4160-8631

India - Pune
Tel: 91-20-4121-0141

Japan - Osaka
Tel: 81-6-6152-7160

Japan - Tokyo
Tel: 81-3-6880-3770

Korea - Daegu
Tel: 82-53-744-4301

Korea - Seoul
Tel: 82-2-554-7200

Malaysia - Kuala Lumpur
Tel: 60-3-7651-7906

Malaysia - Penang
Tel: 60-4-227-8870

Philippines - Manila
Tel: 63-2-634-9065

Singapore
Tel: 65-6334-8870

Taiwan - Hsin Chu
Tel: 886-3-577-8366

Taiwan - Kaohsiung
Tel: 886-7-213-7830

Taiwan - Taipei
Tel: 886-2-2508-8600

Thailand - Bangkok
Tel: 66-2-694-1351

Vietnam - Ho Chi Minh
Tel: 84-28-5448-2100

EUROPE

Austria - Wels
Tel: 43-7242-2244-39
Fax: 43-7242-2244-393

Denmark - Copenhagen
Tel: 45-4485-5910
Fax: 45-4485-2829

Finland - Espoo
Tel: 358-9-4520-820

France - Paris
Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany - Garching
Tel: 49-8931-9700

Germany - Haan
Tel: 49-2129-3766400

Germany - Heilbronn
Tel: 49-7131-72400

Germany - Karlsruhe
Tel: 49-721-625370

Germany - Munich
Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Germany - Rosenheim
Tel: 49-8031-354-560

Israel - Ra'anana
Tel: 972-9-744-7705

Italy - Milan
Tel: 39-0331-742611
Fax: 39-0331-466781

Italy - Padova
Tel: 39-049-7625286

Netherlands - Drunen
Tel: 31-416-690399
Fax: 31-416-690340

Norway - Trondheim
Tel: 47-7288-4388

Poland - Warsaw
Tel: 48-22-3325737

Romania - Bucharest
Tel: 40-21-407-87-50

Spain - Madrid
Tel: 34-91-708-08-90
Fax: 34-91-708-08-91

Sweden - Gothenberg
Tel: 46-31-704-60-40

Sweden - Stockholm
Tel: 46-8-5090-4654

UK - Wokingham
Tel: 44-118-921-5800
Fax: 44-118-921-5820