

Horn Driver Application Note

Author: John Humenick
Microchip Technology Inc.

INTRODUCTION

Microchip CO and Smoke Detector products typically include a piezoelectric horn driver which uses the same circuit architecture as Microchip's Horn Driver products. These horn drivers are used to drive 2-terminal and 3-terminal piezoelectric horns (buzzers) for any application, but typically for smoke and CO detectors. UL217 and EN14604 require a minimum output sound pressure level, SPL, of 85 dBA at 10 ft or 3m. These horn drivers provide the necessary electrical drive to properly selected horns to meet these specifications.

This application note will provide information for both the 2-terminal and 3-terminal application.

The RE46C100 will be used throughout this application note but this applies to all products with horn drivers.

2-TERMINAL HORN DRIVER

The basic horn driver circuit is a digital RC oscillator shown in [Figure 1](#).

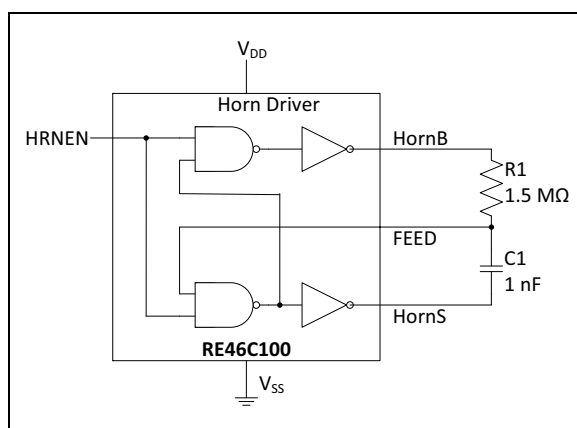


FIGURE 1: Schematic of Basic Horn Driver.

With HRNEN low, both HB and HS are at a logic low. With HRNEN at a logic high, the oscillator function is enabled. Complimentary square waves are output at HB and HS. The FEED pin-switching threshold is set to one-half the supply voltage. If the FEED pin threshold is offset from one-half supply, the output square wave at HB and HS will not have a 50% duty cycle, which is important for achieving the 85 dBA SPL.

When HRNEN is switched high, FEED is initially low, the capacitor C1 is discharged and HB switches high. With HB switched high, capacitor C1 begins charging to one-half the supply voltage. When the FEED pin voltage reaches one-half supply, HB switches low and HS switches high. The FEED pin is now one-half the supply voltage above V_{DD} , e.g., FEED = 13.5V when V_{DD} = 9V. The capacitor C1 now begins to discharge down to one-half the supply voltage. When the FEED pin voltage reaches one-half supply, HB switches high and HS switches low. The FEED pin is now one-half the supply voltage below V_{SS} , e.g., FEED = -4.5V when V_{DD} = 9V and the charging cycle starts over. The horn driver voltage effectively doubles the supply voltage, V_{DD} , used to drive the horn when compared to a single ended horn drive.

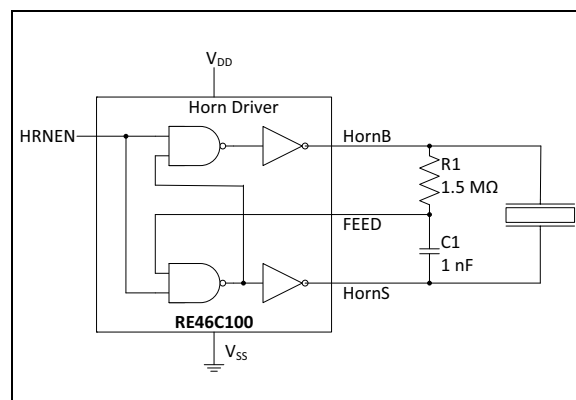


FIGURE 2: 2-Terminal Horn Driver with Piezoelectric Horn.

The frequency of operation is given by $f = 1/(2.2 \cdot R1 \cdot C1)$. For the values shown in [Figure 2](#), the square wave frequency is 303 Hz. If R1 is reduced to about 130 kΩ, the frequency increases to 3500 Hz. [Figure 3](#) shows a plot of the equation versus $1/R1$ and the actual performance of the RE46C100 with and without the horn.

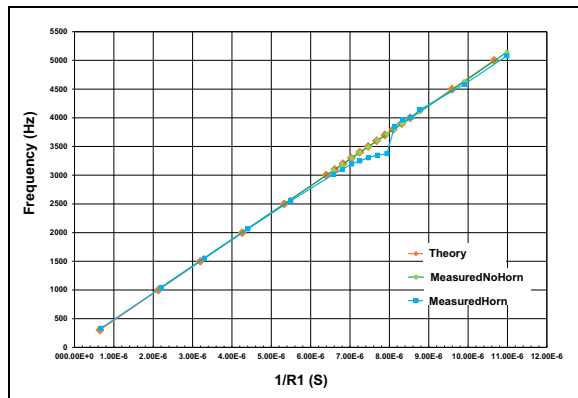


FIGURE 3: Frequency vs. $1/R1$.

When the piezoelectric horn is connected in the circuit (see Figure 2), it loads the drive circuit as the frequency is tuned closer to the horn resonant frequency. The model for a 2-terminal horn is shown in Figure 4. At series resonance, the horn exhibits its lowest resistance. The worst case on resistance of the HB and HS outputs is about 31Ω at 9V. This on resistance produces a voltage drop for large load currents, which affects the charging and discharging time of the RC network connected between HB and HS.

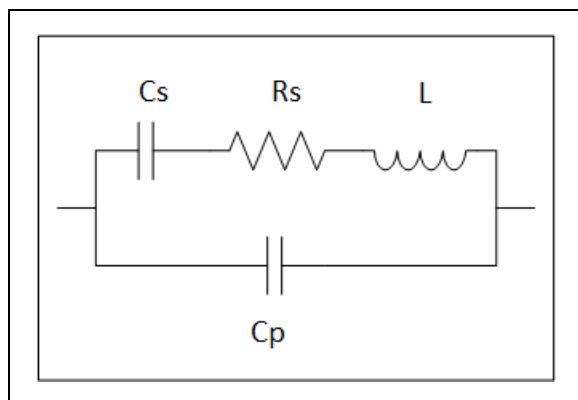


FIGURE 4: 2-Terminal Piezoelectric Horn Electrical Model.

Figure 5 shows the scope traces for the schematic in Figure 2. The horn operates at series resonance, which loads the driver outputs.

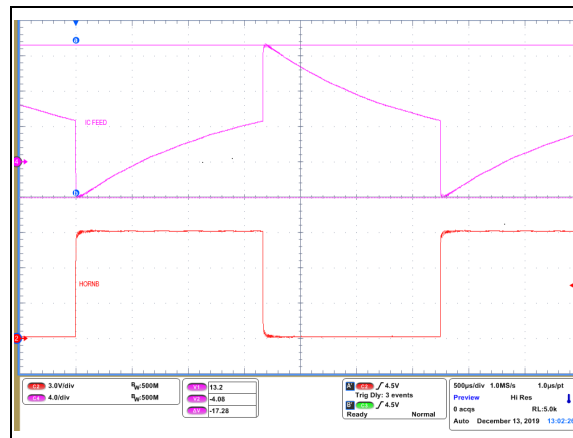


FIGURE 5: Scope Trace for 2-Terminal Operation.

Alternatively, the FEED pin can be driven by a square wave. In Figure 6, a logic level NMOS device is used to level shift a 3.3V square wave to drive the FEED pin. R1 can be increased to reduce the current draw.

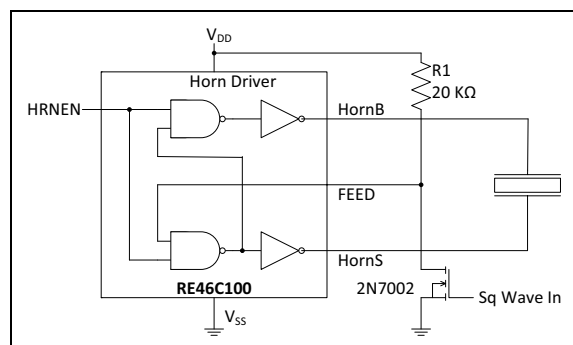


FIGURE 6: 2-Terminal Horn Driver with NMOS Level Shifter.

3-TERMINAL HORN DRIVER

The 3-terminal horn driver is shown in Figure 7. The horn G terminal must connect to the HornB pin and the horn M terminal must connect to the HornS pin. The G terminal is the metal plate where the ceramic material is deposited. The M terminal is the metal film contact on top of the ceramic material. The F terminal of the horn provides a feedback signal that affects the charging and discharging of the capacitor, C1.

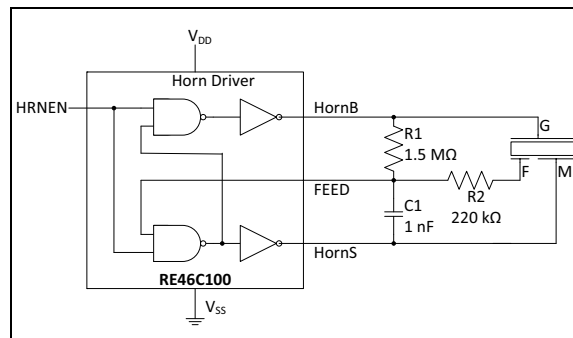
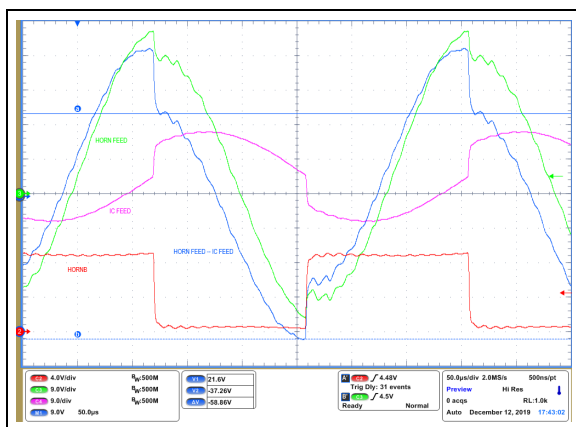


FIGURE 7: 3-Terminal Horn Driver.

At power-up R1 and C1 start the oscillator running. In particular, R1 is chosen to minimize its interaction with the charging/discharging cycle once the oscillator is running at the resonant frequency.

In Figure 8, when HORNB switches low, the initial R1 current is IC FEED/R1, which is approximately 9 μ A (IC FEED = ~13.5V) and the initial R2 current is (HORN FEED – IC FEED)/R2, which is approximately 98.2 μ A ((HORN FEED – IC FEED) = 21.6V). HORN FEED is the horn F terminal voltage. The larger charging/discharging current flowing through R2 controls the charging/discharging cycle for C1.

**FIGURE 8:** 3-Terminal Horn Voltage Waveforms.

The waveforms in Figure 8 show the optimum resonance condition. When HORNB switches, the HORN FEED voltage is at its peak. Finding the best R2*C1 product produces this result. There is no simple equation for calculating this product. It is easier to experimentally adjust the value of C1 and R2 to achieve optimum resonance. Using $R2 \cdot C1 \cdot F0 = 0.75$, where F0 is the resonant frequency of the horn, provides a reasonable initial estimate of the R2 *C1 product.

REFERENCE

1. RE46C100 Data Sheet, "Piezoelectric Horn Driver Circuit", DS20002166B, Microchip Technology Inc, 2014.
2. "AVX Piezoelectric Acoustic Generators", Kyocera.

AN4525

NOTES:

Note the following details of the code protection feature on Microchip products:

- Microchip products meet the specifications contained in their particular Microchip Data Sheet.
 - Microchip believes that its family of products is secure when used in the intended manner, within operating specifications, and under normal conditions.
 - Microchip values and aggressively protects its intellectual property rights. Attempts to breach the code protection features of Microchip product is strictly prohibited and may violate the Digital Millennium Copyright Act.
 - Neither Microchip nor any other semiconductor manufacturer can guarantee the security of its code. Code protection does not mean that we are guaranteeing the product is “unbreakable”. Code protection is constantly evolving. Microchip is committed to continuously improving the code protection features of our products.
-

This publication and the information herein may be used only with Microchip products, including to design, test, and integrate Microchip products with your application. Use of this information in any other manner violates these terms. Information regarding device applications is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. Contact your local Microchip sales office for additional support or, obtain additional support at <https://www.microchip.com/en-us/support/design-help/client-support-services>.

THIS INFORMATION IS PROVIDED BY MICROCHIP “AS IS”. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION INCLUDING BUT NOT LIMITED TO ANY IMPLIED WARRANTIES OF NON-INFRINGEMENT, MERCHANTABILITY, AND FITNESS FOR A PARTICULAR PURPOSE, OR WARRANTIES RELATED TO ITS CONDITION, QUALITY, OR PERFORMANCE.

IN NO EVENT WILL MICROCHIP BE LIABLE FOR ANY INDIRECT, SPECIAL, PUNITIVE, INCIDENTAL, OR CONSEQUENTIAL LOSS, DAMAGE, COST, OR EXPENSE OF ANY KIND WHATSOEVER RELATED TO THE INFORMATION OR ITS USE, HOWEVER CAUSED, EVEN IF MICROCHIP HAS BEEN ADVISED OF THE POSSIBILITY OR THE DAMAGES ARE FORESEEABLE. TO THE FULLEST EXTENT ALLOWED BY LAW, MICROCHIP’S TOTAL LIABILITY ON ALL CLAIMS IN ANY WAY RELATED TO THE INFORMATION OR ITS USE WILL NOT EXCEED THE AMOUNT OF FEES, IF ANY, THAT YOU HAVE PAID DIRECTLY TO MICROCHIP FOR THE INFORMATION.

Use of Microchip devices in life support and/or safety applications is entirely at the buyer’s risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights unless otherwise stated.

For information regarding Microchip’s Quality Management Systems, please visit www.microchip.com/quality.

Trademarks

The Microchip name and logo, the Microchip logo, Adaptec, AnyRate, AVR, AVR logo, AVR Freaks, BesTime, BitCloud, CryptoMemory, CryptoRF, dsPIC, flexPWR, HELDO, IGLOO, JukeBlox, KeeLoq, Klear, LANCheck, LinkMD, maxStylus, maxTouch, MediaLB, megaAVR, Microsemi, Microsemi logo, MOST, MOST logo, MPLAB, OptoLyzer, PIC, picoPower, PICSTART, PIC32 logo, PolarFire, Prochip Designer, QTouch, SAM-BA, SenGenuity, SpyNIC, SST, SST Logo, SuperFlash, Symmetricom, SyncServer, Tachyon, TimeSource, tinyAVR, UNI/O, Vectron, and XMEGA are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

AgileSwitch, APT, ClockWorks, The Embedded Control Solutions Company, EtherSynch, Flashtec, Hyper Speed Control, HyperLight Load, IntelliMOS, Libero, motorBench, mTouch, Powermite 3, Precision Edge, ProASIC, ProASIC Plus, ProASIC Plus logo, QuietWire, SmartFusion, SyncWorld, Temux, TimeCesium, TimeHub, TimePictra, TimeProvider, TrueTime, WinPath, and ZL are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Adjacent Key Suppression, AKS, Analog-for-the-Digital Age, Any Capacitor, AnyIn, AnyOut, Augmented Switching, BlueSky, BodyCom, CodeGuard, CryptoAuthentication, CryptoAutomotive, CryptoCompanion, CryptoController, dsPICDEM, dsPICDEM.net, Dynamic Average Matching, DAM, ECAN, Espresso T1S, EtherGREEN, GridTime, IdealBridge, In-Circuit Serial Programming, ICSP, INICnet, Intelligent Paralleling, Inter-Chip Connectivity, JitterBlocker, Knob-on-Display, maxCrypto, maxView, memBrain, Mindi, MiWi, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, MultiTRAK, NetDetach, NVM Express, NVMe, Omniscient Code Generation, PICDEM, PICDEM.net, PICKit, PICTail, PowerSmart, PureSilicon, QMatrix, REAL ICE, Ripple Blocker, RTAX, RTG4, SAM-ICE, Serial Quad I/O, simpleMAP, SimpliPHY, SmartBuffer, SmartHLS, SMART-I.S., storClad, SQL, SuperSwitcher, SuperSwitcher II, Switchtec, SynchroPHY, Total Endurance, TSHARC, USBCheck, VariSense, VectorBlox, VeriPHY, ViewSpan, WiperLock, XpressConnect, and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

The Adaptec logo, Frequency on Demand, Silicon Storage Technology, Symmcom, and Trusted Time are registered trademarks of Microchip Technology Inc. in other countries.

GestIC is a registered trademark of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies.

© 2022, Microchip Technology Incorporated and its subsidiaries.

All Rights Reserved.

ISBN: 978-1-6683-0200-2

Worldwide Sales and Service

AMERICAS

Corporate Office
2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support:
<http://www.microchip.com/support>
Web Address:
www.microchip.com

Atlanta
Duluth, GA
Tel: 678-957-9614
Fax: 678-957-1455

Austin, TX
Tel: 512-257-3370

Boston
Westborough, MA
Tel: 774-760-0087
Fax: 774-760-0088

Chicago
Itasca, IL
Tel: 630-285-0071
Fax: 630-285-0075

Dallas
Addison, TX
Tel: 972-818-7423
Fax: 972-818-2924

Detroit
Novi, MI
Tel: 248-848-4000

Houston, TX
Tel: 281-894-5983

Indianapolis
Noblesville, IN
Tel: 317-773-8323
Fax: 317-773-5453
Tel: 317-536-2380

Los Angeles
Mission Viejo, CA
Tel: 949-462-9523
Fax: 949-462-9608
Tel: 951-273-7800

Raleigh, NC
Tel: 919-844-7510

New York, NY
Tel: 631-435-6000

San Jose, CA
Tel: 408-735-9110
Tel: 408-436-4270

Canada - Toronto
Tel: 905-695-1980
Fax: 905-695-2078

ASIA/PACIFIC

Australia - Sydney
Tel: 61-2-9868-6733

China - Beijing
Tel: 86-10-8569-7000

China - Chengdu
Tel: 86-28-8665-5511

China - Chongqing
Tel: 86-23-8980-9588

China - Dongguan
Tel: 86-769-8702-9880

China - Guangzhou
Tel: 86-20-8755-8029

China - Hangzhou
Tel: 86-571-8792-8115

China - Hong Kong SAR
Tel: 852-2943-5100

China - Nanjing
Tel: 86-25-8473-2460

China - Qingdao
Tel: 86-532-8502-7355

China - Shanghai
Tel: 86-21-3326-8000

China - Shenyang
Tel: 86-24-2334-2829

China - Shenzhen
Tel: 86-755-8864-2200

China - Suzhou
Tel: 86-186-6233-1526

China - Wuhan
Tel: 86-27-5980-5300

China - Xian
Tel: 86-29-8833-7252

China - Xiamen
Tel: 86-592-2388138

China - Zhuhai
Tel: 86-756-3210040

ASIA/PACIFIC

India - Bangalore
Tel: 91-80-3090-4444

India - New Delhi
Tel: 91-11-4160-8631

India - Pune
Tel: 91-20-4121-0141

Japan - Osaka
Tel: 81-6-6152-7160

Japan - Tokyo
Tel: 81-3-6880-3770

Korea - Daegu
Tel: 82-53-744-4301

Korea - Seoul
Tel: 82-2-554-7200

Malaysia - Kuala Lumpur
Tel: 60-3-7651-7906

Malaysia - Penang
Tel: 60-4-227-8870

Philippines - Manila
Tel: 63-2-634-9065

Singapore
Tel: 65-6334-8870

Taiwan - Hsin Chu
Tel: 886-3-577-8366

Taiwan - Kaohsiung
Tel: 886-7-213-7830

Taiwan - Taipei
Tel: 886-2-2508-8600

Thailand - Bangkok
Tel: 66-2-694-1351

Vietnam - Ho Chi Minh
Tel: 84-28-5448-2100

EUROPE

Austria - Wels
Tel: 43-7242-2244-39
Fax: 43-7242-2244-393

Denmark - Copenhagen
Tel: 45-4485-5910
Fax: 45-4485-2829

Finland - Espoo
Tel: 358-9-4520-820

France - Paris
Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany - Garching
Tel: 49-8931-9700

Germany - Haan
Tel: 49-2129-3766400

Germany - Heilbronn
Tel: 49-7131-72400

Germany - Karlsruhe
Tel: 49-721-625370

Germany - Munich
Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Germany - Rosenheim
Tel: 49-8031-354-560

Israel - Ra'anana
Tel: 972-9-744-7705

Italy - Milan
Tel: 39-0331-742611
Fax: 39-0331-466781

Italy - Padova
Tel: 39-049-7625286

Netherlands - Drunen
Tel: 31-416-690399
Fax: 31-416-690340

Norway - Trondheim
Tel: 47-7288-4388

Poland - Warsaw
Tel: 48-22-3325737

Romania - Bucharest
Tel: 40-21-407-87-50

Spain - Madrid
Tel: 34-91-708-08-90
Fax: 34-91-708-08-91

Sweden - Gothenberg
Tel: 46-31-704-60-40

Sweden - Stockholm
Tel: 46-8-5090-4654

UK - Wokingham
Tel: 44-118-921-5800
Fax: 44-118-921-5820