

Application Guidelines for the Microchip Constant On-Time Regulators with Internal Ripple Injection

Author: Paolo Nora, Victor Uzum Microchip Technology Inc.

INTRODUCTION

Buck Switch-Mode Power Supplies are popular solutions for today's customer POL applications. The main control mode architecture types are: voltage-mode, current-mode and Constant On-Time (COT) control mode.

The ripple-based COT control architecture is more and more popular among customers due to its very simple control loop design, fast transient response (due to wide bandwidth), while achieving a relatively constant switching frequency and high efficiency at light loads, and implemented with little additional design effort.

CONSTANT ON-TIME CONTROL ARCHITECTURE

COT is a ripple-based control mode. The output regulation is achieved by comparing the falling slope of the output voltage to a threshold. As illustrated in Figure 1, when the output voltage waveform V_O is crossing the regulation threshold V_{REF} , switch HS is activated (the SR latch is set).

At the same time, an internal I/C timer starts and generates a RESET pulse to the latch after a certain time, TON. Therefore, the high-side switch will be activated for a fixed time, equal to TON, which is fixed by the I_T/C_{TON} slope across the timing capacitor C_{TON}, and by the value of threshold V_{TH}. Since all the parameters determining T_{ON} are constant, the ON-time of HS is also constant, which is why the basic form of this type of control is called "Constant ON-Time". It should be noted that the duration of the RESET pulse to the SR latch might be stretched as needed by the "Min. T_{OFF}" one-shot to enforce a minimum duration of the OFF time. This is needed, for example, to replenish the bootstrap capacitor for the high-side driver (if the HS switch is an N-channel MOSFET driven by a bootstrapped driver), or for measuring the current across the R_{DS(ON)} of the low-side switch LS, as in the case of many regulators listed below.

Indeed, if the output voltage waveform is still below the regulation threshold V_{REF} after the minimum T_{OFF} has expired, the COT regulator immediately reacts by triggering another T_{ON} pulse. This fast reaction to a sagging output voltage, a key factor in load transient response, is the main benefit of COT control.

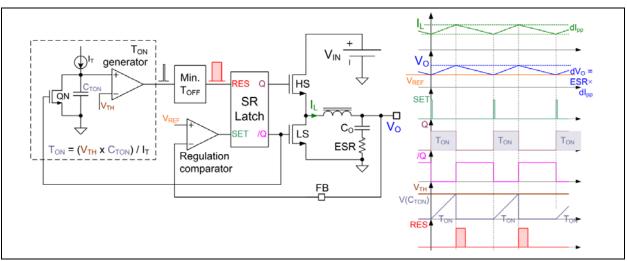


FIGURE 1: Constant On-Time Control Architecture.

Despite its uncontestable advantages, this control scheme has an important drawback. The output voltage ripple must be large enough to reliably trigger the comparator and, most importantly, the phase of the output ripple must closely match the inductor current ripple component, meaning that the output voltage capacitor ESR must be quite large.

Many authors have performed a detailed analysis of the stability constraints for COT due to the output capacitor ESR [Redl, Sun, Lee]. They all conclude that the stability constraint is:

EQUATION 1:

$$\frac{T_{ON}}{2} < ESR \times C_O$$

Since large output ripple is not desirable in most customer applications, two main solutions can be implemented to provide a large enough ripple on the feedback path without increasing the output voltage ripple: ripple injection and Emulated Ripple Mode (ERM). For a detailed description of COT architecture and ripple injection techniques, refer to the documents and the tutorial presentations available on the Microchip website.

RIPPLE INJECTION TECHNIQUES

There are various techniques for feedback ripple injection in COT regulators, listed below.

LARGE ESR OUTPUT CAPACITOR (OR A RESISTOR IN SERIES WITH THE OUTPUT CAPACITOR)

This solution is not usually desirable, since low output voltage ripple is one of the most frequent constraints in customer applications. In addition, this method is sensitive to output noise, since it is translated into feedback ripple. Usually, low ESR ceramic output capacitors are recommended for this type of regulator because of their good high-frequency characteristics and output ripple attenuation performance.

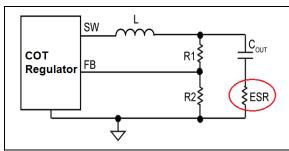


FIGURE 2: Increasing the Feedback Ripple by Increasing the Output Capacitor ESR.

A FEED-FORWARD CAPACITOR IN PARALLEL WITH THE TOP RESISTOR OF THE FEEDBACK DIVIDER

This solution can be applied if the time constant of the output capacitor is still adequate for stable operation, but its amplitude at the FB pin is too shallow for jitter-free operation. In this case the full amplitude of the output ripple can be recovered by feeding it directly to the feedback path. The feed forward capacitor bypasses high-frequency ripple directly to the FB pin and ensures a phase boost around the middle of the relevant bandwidth.

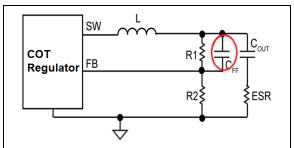


FIGURE 3: Feeding the Output Ripple to the FB Path without Increasing the Output Voltage Ripple.

A SERIES RC CELL ADDED BETWEEN THE SWITCH NODE AND THE FEEDBACK PATH

This solution is necessary if the output capacitor ESR is no longer sufficient to achieve stability. This is the case when ceramic output capacitors are used. In this case, the in-phase ripple must be created using the Ri-Ci network shown in the picture below. The current through Ri is almost a square wave with no DC component (blocked by Ci) and it is integrated across capacitor C_{FF} to generate a triangular wave shape. Care must be taken because C_{FF} also bypasses the entire "out-of-phase" output ripple to the feedback pin, and the self-injected "in-phase" ripple must be large enough to overcome the output ripple.

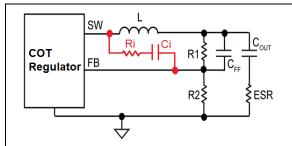


FIGURE 4: Injected Ripple from the SW Node using a Series RC Cell.

INTERNAL RIPPLE INJECTION

In case of low input voltage, low power DC-DC converters using low ESR ceramic output capacitors, the ripple injection components (feed-forward capacitor and the series injection RC cell) are frequently integrated on the regulator die.

This is convenient for customer applications, since the number of external components needed for regulator integration is lower. Additionally, the ripple injection components are already dimensioned for stable loop performance, and for the best compromise between ripple amplitude, the line regulation and the transient response time.

However, to make monolithic integration practical, the value of the DC blocking capacitor is typically limited to some picofarads. Therefore, even if the switching frequency is in the MHz range, the values of Ri and the feedback resistors must be high.

In case of fixed output voltage versions, the feedback resistors are also integrated in the regulator package. That further reduces the number of external components.

Since the switching frequency is internally fixed, a limited range of inductors and a minimum output capacitance are typically suggested for these monolithic regulators to avoid any possible stability issues in customer applications.

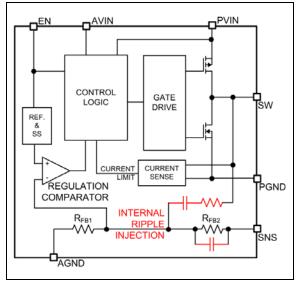


FIGURE 5: Internal Ripple Injection Network Used for Low-power COT Regulators.

MICROCHIP REGULATORS WITH INTERNAL RIPPLE INJECTION

There are many buck hysteretic COT regulators with internal ripple injection in the Microchip portfolio, refer to Table 1

TABLE 1: MICROCHIP BUCK COT REGULATORS WITH INTERNAL RIPPLE REJECTION

Product	No. of Outputs	Input Min Voltage (V)	Input Max Voltage (V)	Switching Frequency (Hz)	VFB (V) (adj.)
MIC23158	2	2.7	5.5	3000	0.62
MIC23159	2	2.7	5.5	3000	0.62
MIC23250	2	2.7	5.5	4000	0.72
MIC23254	2	2.5	5.5	4000	N.A. ⁽ 1)
MIC23030	1	2.7	5.5	8000	0.62
MIC23031	1	2.7	5.5	4000	0.62
MIC23050	1	2.7	5.5	4000	N.A. ⁽ 1)
MIC23051	1	2.7	5.5	4000	N.A. ⁽ 1)
MIC23150	1	2.7	5.5	4000	N.A. ⁽ 1)
MIC23153	1	2.7	5.5	4000	0.62
MIC23155	1	2.7	5.5	3000	0.62
MIC23201	1	2.7	5.5	2000	0.62
MIC23303	1	2.9	5.5	4000	0.62
MIC4930	1	2.7	5.5	3300	0.625
MIC4950	1	2.7	5.5	3300	0.625
MIC23603	1	2.9	5.5	4000	0.62
MIC23450	3	2.7	5.5	3000	0.62
MIC23451	3	2.7	5.5	3000	0.62

Note 1: N.A.: adjustable version not available; only fixed output voltage options are offered.

DESIGN CONSTRAINTS FOR MICROCHIP INTERNAL RIPPLE INJECTION REGULATORS

For all COT regulators with internal ripple injection (MIC23XXX and MIC49XX), precise indications related to design application rules are provided in the corresponding data sheets (all documents can be reviewed and downloaded from the Microchip website at http://www.microchip.com).

For all adjustable output voltage versions, recommended values for feedback divider resistors are clearly specified (usually hundreds of kiloohms for both top and bottom resistors). For the fixed output voltage versions, these feedback resistors are inside the regulator package, so they cannot be changed by the end user.

One common recommendation for feedback voltage resistor divider values show in Table 2.

TABLE 2: TYPICALLY RECOMMENDED FEEDBACK RESISTOR VALUES

V _{OUT}	R ₁	R ₂
1.2V	274 kΩ	294 kΩ
1.5V	316 kΩ	226 kΩ
1.8V	301 kΩ	160 kΩ
2.5V	316 kΩ	105 kΩ
3.3V	309 kΩ	71.5 kΩ

The typically recommended feedback resistor values table is applicable to regulators like MIC4930, MIC4950, MIC23450, MIC23451 and MIC23153.

Some of the data sheets also indicate an optimum range for the external feed-forward capacitors (usually a few tens of picofarads) if they are not already included in the regulator internal circuitry.

The same documents also specify the optimal ranges for the external inductors used in the buck step down topology (usually between 0.47 μ H and 4.7 μ H), and the recommended input/output capacitor types and values

Designers must pay attention to all application recommendations and implement them in their designs. Otherwise, they may encounter stability issues, or the ripple fed into the feedback path might not be large enough to ensure optimal functionality of the COT control loop.

The internal ripple injection network is typically sufficient for the desired ripple on the feedback path, if the recommended divider resistors and feed-forward capacitor are used. If significantly lower feedback divider resistors and/or a higher feed-forward capacitor are used, the amount of ripple at the feedback pin might not be sufficient for stable regulator operation. In this case, external ripple injection is needed. This is accomplished by connecting a series RC circuit between the SW and the FB regulator pins and placing a feed-forward capacitor in parallel with the top resistor of the feedback resistive divider (see Figure 4).

The injected ripple is calculated using Equation 2:

EQUATION 2:

$$\Delta V_{FB(pp)} = V_{IN} \times K_{DIV} \times D \times (1-D) \times \frac{1}{f_{SW} \times \tau}$$

where:

EQUATION 3:

$$K_{DIV} = \langle R_1 \parallel R_2 \rangle / (R_{INJ} + R_1 \parallel R_2)$$

EQUATION 4:

$$D = V_{OUT}/V_{IN} = DutyCycle$$

V_{IN} = Input Voltage, V_{OUT} = Output Voltage

EQUATION 5:

$$\tau \equiv (R_1 \parallel R_2 \parallel R_{inj}) \times C_{FF}$$

In the derivation of Equation 2, it is assumed that the condition expressed by Equation 6 is satisfied:

EQUATION 6:

$$\frac{1}{f_{SW} \times \tau} \ll 1$$

where f_{SW} = Switching Frequency.

Please note that the external ripple injection network and feedback network impedance levels must be set low enough to override the effects of the internal ripple injection.

PRACTICAL EXAMPLE (MIC4930/50)

The MIC4930/50 are Microchip buck regulators that feature internal ripple injection (see Figure 5). The components used for their internal ripple injection network are R_{INJ} = 360 k Ω and C_{INJ} = 1.3 pF.

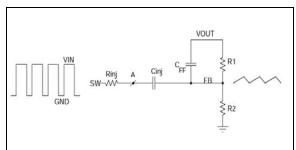


FIGURE 6: MIC4930/50 Internal Injection Path from the SW Node to the FB Pin.

The A node DC voltage is equal to V_{OUT} , because the RC network is the low pass type. This can be better understood by considering that C_{INJ} is a DC blocking capacitor, so no net DC current can flow through R_{INJ} in steady-state. Therefore, the DC (average) values at node SW and at node A must be equal, and the DC value (average) of node SW is D x V_{IN} = V_{OUT} (assuming a loss-less inductor). So, when SW voltage is equal to V_{IN} , the current injected in the feed-forward capacitor (C_{FF}) is calculated in Equation 7 (neglecting the small amount of current flowing through R_1 and R_2).

EQUATION 7:

$$(V_{IN} - V_{OUT})/R_{INJ}$$

The peak-to-peak amplitude of the voltage ripple injected into the feedback node will then be:

EQUATION 8:

$$\Delta V_{FB(pp)} = (V_{IN} - V_{OUT}) / R_{INJ} \times \frac{T_{ON}}{C_{FF}}$$

where T_{ON} is the measured regulator ON time. It can be shown that Equation 2 and Equation 8 yield the same result by using Equations 3, 4 and 5.

Calculating the feedback ripple amplitude for a particular use case (V_{IN} = 5.0V, V_{OUT} = 1.8V, I_{OUT} = 1A, C_{IN} = C_{OUT} = 10uF and C_{FF} = 22 pF), the result is 48 mV_{PP}, as the measured T_{ON} is 119 ns.

In order to confirm the theoretical expected value, the feedback ripple amplitude can be measured using a differential oscilloscope probe (usually less than 1 pF differential capacitance) to avoid adding a higher capacitance in parallel with the feedback path by using

a normal oscilloscope probe. Nevertheless, the parasitic capacitances on the board will still affect the measured result.

For this particular use case, the measured feedback ripple is 46 mVpp for MIC4930, and 47 mV $_{\rm PP}$ for MIC4950, which is close to the theoretically predicted value

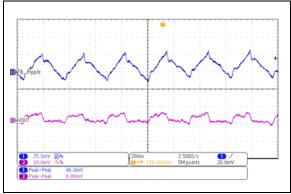


FIGURE 7: MIC4930 Feedback Ripple Amplitude for $V_{IN} = 5.0V$, $V_{OUT} = 1.8V$, $I_{OUT} = 1A$, $C_{FF} = 22$ pF.

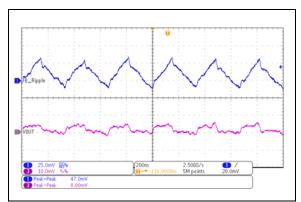


FIGURE 8: MIC4950 Feedback Ripple Amplitude for $V_{IN} = 5.0V$, $V_{OUT} = 1.8V$, $I_{OUT} = 1A$, $C_{FF} = 22pF$.

AN2526

REFERENCES

- MIC23158/59, MIC23250/54, MIC23030/31, MIC23150/51, MIC23150/53/55, MIC23201, MIC23303, MIC23450/51, MIC23603, MIC4930/50 Microchip data sheets.
- 2. Paolo Nora and Surya Talari "Understanding and Designing a Switching Power Supply with Adaptive COT Architecture" 20096 PC6 Masters 2016.
- Feng Yu, Fred C. Lee, Paolo Mattavelli "A Small Signal Model for V2 Control with Composite Output Capacitors Based on Describing Function approach", Energy Conversion Congress and Exposition (ECCE), 2011 IEEE.
- 4. Richard Redl, Jian Sun "Ripple Based Control of Switching Regulators An Overview", IEEE Power Electronics, Vol. 24, No. 12, Dec 2009.
- Jinping Wang, Jianping Xu, Bocheng Bao -"Analysis of Pulse Bursting Phenomenon in Constant-On-Time Controlled Buck Converter", IEEE Industrial Electronics, Vol. 58, No.12, Dec. 2011.
- 6. 20096 PC6 Simplify Your Buck Converter Design with Constant-On-Time Control.

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights unless otherwise stated.

Microchip received ISO/TS-16949:2009 certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona; Gresham, Oregon and design centers in California and India. The Company's quality system processes and procedures are for its PIC® MCUs and dsPIC® DSCs, KEELOQ® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.

QUALITY MANAGEMENT SYSTEM CERTIFIED BY DNV = ISO/TS 16949=

Trademarks

The Microchip name and logo, the Microchip logo, AnyRate, AVR, AVR logo, AVR Freaks, BeaconThings, BitCloud, CryptoMemory, CryptoRF, dsPIC, FlashFlex, flexPWR, Heldo, JukeBlox, KEELOQ, KEELOQ logo, Kleer, LANCheck, LINK MD, maXStylus, maXTouch, MediaLB, megaAVR, MOST, MOST logo, MPLAB, OptoLyzer, PIC, picoPower, PICSTART, PIC32 logo, Prochip Designer, QTouch, RightTouch, SAM-BA, SpyNIC, SST, SST Logo, SuperFlash, tinyAVR, UNI/O, and XMEGA are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

ClockWorks, The Embedded Control Solutions Company, EtherSynch, Hyper Speed Control, HyperLight Load, IntelliMOS, mTouch, Precision Edge, and Quiet-Wire are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Adjacent Key Suppression, AKS, Analog-for-the-Digital Age, Any Capacitor, AnyIn, AnyOut, BodyCom, chipKIT, chipKIT logo, CodeGuard, CryptoAuthentication, CryptoCompanion, CryptoController, dsPICDEM, dsPICDEM.net, Dynamic Average Matching, DAM, ECAN, EtherGREEN, In-Circuit Serial Programming, ICSP, Inter-Chip Connectivity, JitterBlocker, KleerNet, KleerNet logo, Mindi, MiWi, motorBench, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, MultiTRAK, NetDetach, Omniscient Code Generation, PICDEM, PICDEM.net, PICkit, PICtail, PureSilicon, QMatrix, RightTouch logo, REAL ICE, Ripple Blocker, SAM-ICE, Serial Quad I/O, SMART-I.S., SQI, SuperSwitcher, SuperSwitcher II, Total Endurance, TSHARC, USBCheck, VariSense, ViewSpan, WiperLock, Wireless DNA, and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

Silicon Storage Technology is a registered trademark of Microchip Technology Inc. in other countries.

GestIC is a registered trademark of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies

© 2017, Microchip Technology Incorporated, All Rights Reserved. ISBN: 978-1-5224-2175-7



Worldwide Sales and Service

AMERICAS

Corporate Office 2355 West Chandler Blvd. Chandler, AZ 85224-6199 Tel: 480-792-7200

Fax: 480-792-7277 Technical Support:

http://www.microchip.com/ support

Web Address: www.microchip.com

Atlanta

Duluth, GA Tel: 678-957-9614 Fax: 678-957-1455

Austin, TX Tel: 512-257-3370

Boston

Westborough, MA Tel: 774-760-0087 Fax: 774-760-0088

Chicago

Tel: 630-285-0071 Fax: 630-285-0075

Dallas

Addison, TX Tel: 972-818-7423 Fax: 972-818-2924

Detroit Novi, MI

Tel: 248-848-4000

Houston, TX Tel: 281-894-5983

Indianapolis

Noblesville, IN Tel: 317-773-8323 Fax: 317-773-5453 Tel: 317-536-2380

Los Angeles

Mission Viejo, CA Tel: 949-462-9523 Fax: 949-462-9608 Tel: 951-273-7800

Raleigh, NC Tel: 919-844-7510

lel: 919-844-7510

Tel: 631-435-6000

San Jose, CA Tel: 408-735-9110 Tel: 408-436-4270

Canada - Toronto Tel: 905-695-1980 Fax: 905-695-2078

ASIA/PACIFIC

Asia Pacific Office Suites 3707-14, 37th Floor Tower 6, The Gateway

Harbour City, Kowloon

Hong Kong Tel: 852-2943-5100 Fax: 852-2401-3431

Australia - Sydney Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

China - Beijing Tel: 86-10-8569-7000 Fax: 86-10-8528-2104

China - Chengdu Tel: 86-28-8665-5511 Fax: 86-28-8665-7889

China - Chongqing Tel: 86-23-8980-9588 Fax: 86-23-8980-9500

China - Dongguan Tel: 86-769-8702-9880

China - Guangzhou Tel: 86-20-8755-8029

China - Hangzhou Tel: 86-571-8792-8115 Fax: 86-571-8792-8116

China - Hong Kong SAR Tel: 852-2943-5100 Fax: 852-2401-3431

China - Nanjing Tel: 86-25-8473-2460 Fax: 86-25-8473-2470

China - Qingdao Tel: 86-532-8502-7355 Fax: 86-532-8502-7205

China - Shanghai Tel: 86-21-3326-8000 Fax: 86-21-3326-8021

China - Shenyang Tel: 86-24-2334-2829

Fax: 86-24-2334-2393 **China - Shenzhen** Tel: 86-755-8864-2200

Fax: 86-755-8203-1760 **China - Wuhan** Tel: 86-27-5980-5300

Fax: 86-27-5980-5118 China - Xian

Tel: 86-29-8833-7252 Fax: 86-29-8833-7256

ASIA/PACIFIC

China - Xiamen Tel: 86-592-2388138 Fax: 86-592-2388130

China - Zhuhai Tel: 86-756-3210040 Fax: 86-756-3210049

India - Bangalore Tel: 91-80-3090-4444 Fax: 91-80-3090-4123

India - New Delhi Tel: 91-11-4160-8631 Fax: 91-11-4160-8632

India - Pune Tel: 91-20-3019-1500

Japan - Osaka Tel: 81-6-6152-7160 Fax: 81-6-6152-9310

Japan - Tokyo Tel: 81-3-6880- 3770 Fax: 81-3-6880-3771

Korea - Daegu Tel: 82-53-744-4301 Fax: 82-53-744-4302

Korea - Seoul Tel: 82-2-554-7200 Fax: 82-2-558-5932 or 82-2-558-5934

Malaysia - Kuala Lumpur Tel: 60-3-6201-9857 Fax: 60-3-6201-9859

Malaysia - Penang Tel: 60-4-227-8870 Fax: 60-4-227-4068

Philippines - Manila Tel: 63-2-634-9065 Fax: 63-2-634-9069

Singapore

Tel: 65-6334-8870 Fax: 65-6334-8850

Taiwan - Hsin Chu Tel: 886-3-5778-366 Fax: 886-3-5770-955

Taiwan - Kaohsiung Tel: 886-7-213-7830

Taiwan - Taipei Tel: 886-2-2508-8600 Fax: 886-2-2508-0102

Thailand - Bangkok Tel: 66-2-694-1351 Fax: 66-2-694-1350

EUROPE

Austria - Wels Tel: 43-7242-2244-39 Fax: 43-7242-2244-393

Denmark - Copenhagen Tel: 45-4450-2828 Fax: 45-4485-2829

Finland - Espoo Tel: 358-9-4520-820

France - Paris
Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

France - Saint Cloud Tel: 33-1-30-60-70-00

Germany - Garching Tel: 49-8931-9700 **Germany - Haan** Tel: 49-2129-3766400

Germany - Heilbronn Tel: 49-7131-67-3636

Germany - Karlsruhe Tel: 49-721-625370

Germany - Munich Tel: 49-89-627-144-0 Fax: 49-89-627-144-44

Germany - Rosenheim Tel: 49-8031-354-560

Israel - Ra'anana Tel: 972-9-744-7705

Italy - Milan Tel: 39-0331-742611 Fax: 39-0331-466781

Italy - Padova Tel: 39-049-7625286

Netherlands - Drunen Tel: 31-416-690399 Fax: 31-416-690340

Norway - Trondheim Tel: 47-7289-7561

Poland - Warsaw Tel: 48-22-3325737

Romania - Bucharest

Spain - Madrid Tel: 34-91-708-08-90 Fax: 34-91-708-08-91

Sweden - Gothenberg Tel: 46-31-704-60-40

Sweden - Stockholm Tel: 46-8-5090-4654

UK - Wokingham Tel: 44-118-921-5800 Fax: 44-118-921-5820