

REV	CHANGE DESCRIPTION	NAME	DATE
A	Release		02-05-13

Any assistance, services, comments, information, or suggestions provided by SMSC (including without limitation any comments to the effect that the Company's product designs do not require any changes) (collectively, "SMSC Feedback") are provided solely for the purpose of assisting the Company in the Company's attempt to optimize compatibility of the Company's product designs with certain SMSC products. SMSC does not promise that such compatibility optimization will actually be achieved. Circuit diagrams utilizing SMSC products are included as a means of illustrating typical applications; consequently, complete information sufficient for construction purposes is not necessarily given. Although the information has been checked and is believed to be accurate, no responsibility is assumed for inaccuracies. SMSC reserves the right to make changes to specifications and product descriptions at any time without notice.

DOCUMENT DESCRIPTION
Routing Checklist for the LAN8720I, 24-pin QFN Package

 	SMSC 80 Arkay Drive Hauppauge, New York 11788	
	Document Number	Revision
	RC614949	A

Routing Checklist for LAN8720I

Information Particular for the 24-pin QFN Package

LAN8720I QFN Phy Interface:

1. The traces connecting the transmit outputs (TXP, pin 21) & (TXN, pin 20) to the magnetics must be run as differential pairs. The differential impedance should be 100 ohms.
2. The traces connecting the receive inputs (RXP, pin 23) & (RXN, pin 22) from the magnetics must be run as differential pairs. The differential impedance should be 100 ohms.
3. For differential traces running from the LAN controller to the magnetics, SMSC recommends routing these traces on the component side of the PCB with a contiguous digital ground plane on the next layer. This will minimize the use of vias and avoid impedance mismatches by switching PCB layers.
4. Refer to Figure No. 1 for differential pair routing details.
5. The VDD1A/VDD2A power supply should be routed as a mini-plane and can be routed on an internal power plane layer.
6. Refer to Figure No. 2 for VDD1A/VDD2A power plane details.

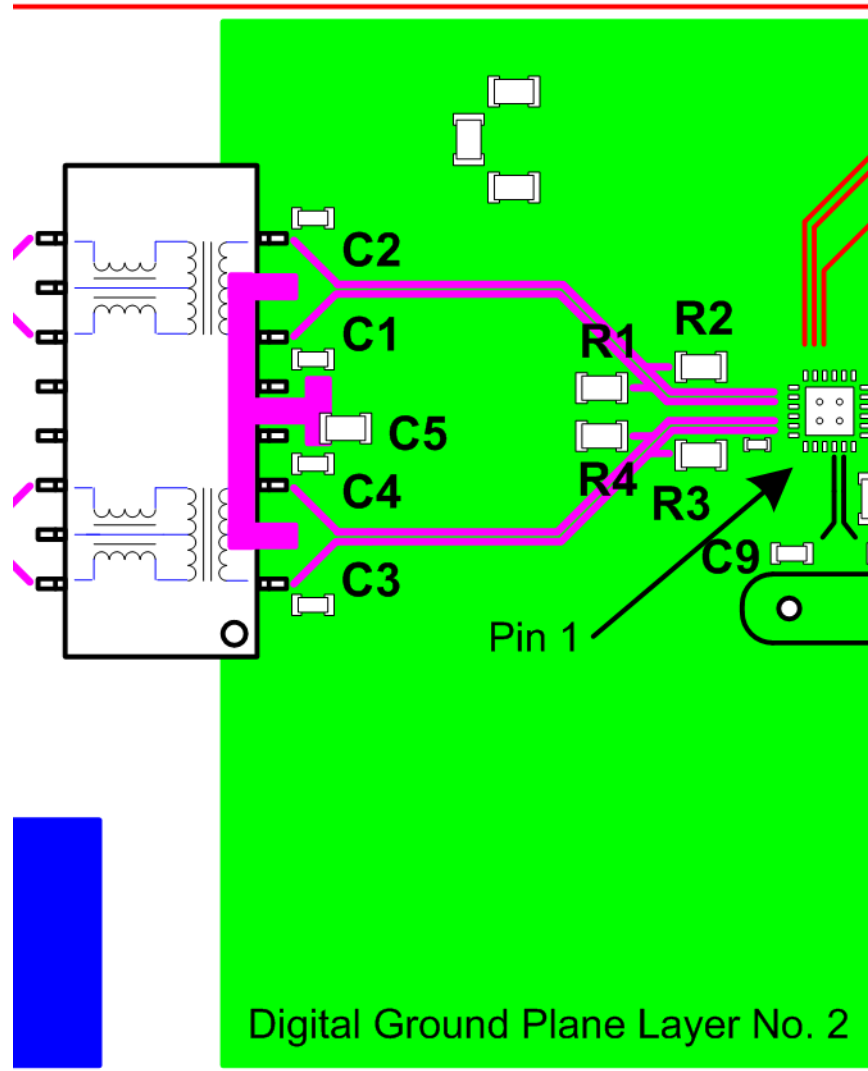


Figure No. 1

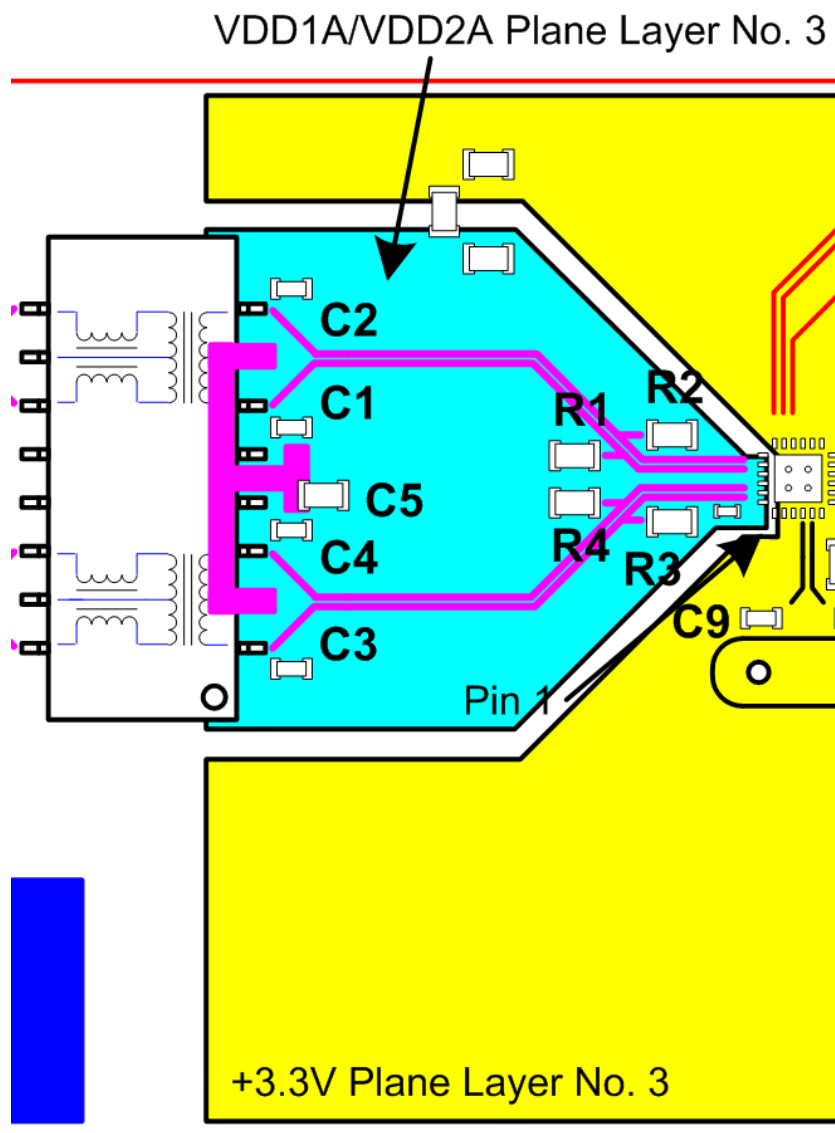


Figure No. 2

LAN8720I QFN Magnetics:

1. The traces connecting the transmit outputs from the magnetics to pins 1 & 2 on the RJ45 connector must be run as differential pairs. Again, the differential impedance should be 100 ohms.
2. The traces connecting the receive inputs on the magnetics from pins 3 & 6 on the RJ45 connector must be run as differential pairs. Again, the differential impedance should be 100 ohms.
3. For differential traces running from the magnetics to the RJ45 connector, SMSC recommends routing these traces on the component side of the PCB with all power planes (including chassis ground) cleared out from under these traces. This will minimize the use of vias and minimize any unwanted noise from coupling into the differential pairs. The plane clear out boundary is usually halfway through the magnetics.

RJ45 Connector:

1. Try to keep all other signals out of the Ethernet front end (RJ45 through the magnetics to the LAN chip). Any noise from other traces may couple into the Ethernet section and cause EMC problems.
2. Also recommended, is the construction of a separate chassis ground that can be easily connected to digital ground at one point. This plane provides the lowest impedance path to earth ground.
3. Refer to Figure No. 3 for Ethernet front end routing details.

No Planes or Traces Underneath Two
Differential Pairs in This Area

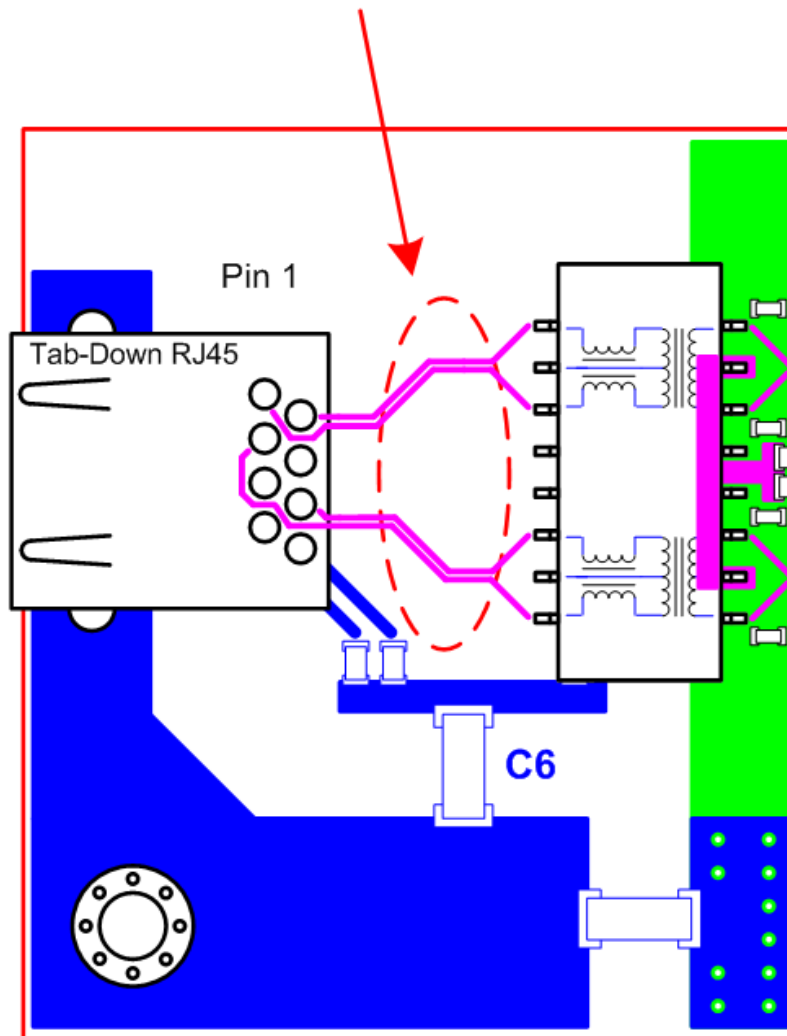


Figure No. 3

Power Supply Connections:

1. Route the (2) VDD1A and VDD2A pins of the LAN8720I QFN directly into a solid, +3.3V power plane (created with a ferrite bead). The pin-to-plane trace should be as short as possible and as wide as possible.
2. In addition, route the (2) VDD1A and VDD2A decoupling capacitors for the LAN8720I QFN power pins as short as possible to each separate power pin. There should be a short, direct copper connection as well as a connection to each power plane (+3.3V & digital ground plane) for each cap.
3. Route the (1) VDDIO pin of the LAN8720I QFN directly into a solid, variable voltage (+1.8V to +3.3V) power plane. The pin-to-plane trace should be as short as possible and as wide as possible.
4. In addition, route the (1) VDDIO decoupling capacitor for the LAN8720I power pin as short as possible to the power pin. There should be a short, direct copper connection as well as a connection to each power plane (power plane & digital ground plane) for the cap.

Ground Connections:

1. The single digital ground pin (pin 25, EDP) on the LAN8720I QFN should be connected directly into a solid, contiguous, internal ground plane. The EDP pad on the component side of the PCB should be connected to the internal digital ground plane with 4 power vias in a 2x2 grid.
2. We recommend that all Ground pins be tied together to the same ground plane. We do not recommend running separate ground planes for any of our LAN products.

VDDCR:

1. The VDDCR pin, pin 6, must be routed with a heavy, wide trace with multiple vias to the single decoupling cap and the single bulk capacitor associated with it. A mini-plane is also acceptable.

Crystal Connections:

1. The routing for the crystal or clock circuitry should be kept as small as possible and as short as possible. Refer to Figure No. 4 below for details.
2. A small ground flood routed under the crystal package on the component layer of PCB may improve the emissions signature. Stitch the flood with multiple vias into the digital ground plane directly below it.
3. The REF_CLK Out Mode is not part of the RMII Specification. Timing in this mode is not compliant with the RMII specification. To ensure proper system operation, a timing analysis of the MAC and LAN8720I must be performed. Some MACs may require a small delay (500 pS – 1.0 nS) to the RXD[1..0] & CRS_DV signals. One method to achieve such a delay is to serpentine the signals from the Phy to the MAC.

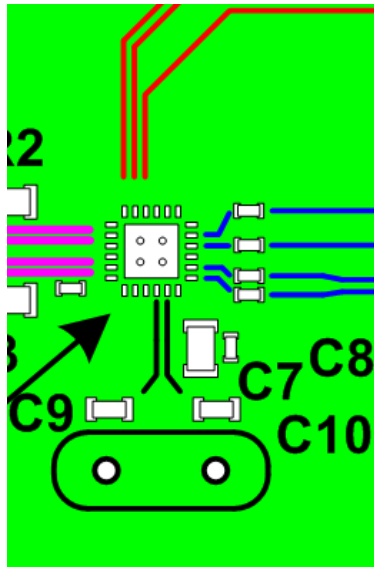


Figure No. 4

Clock Oscillator Connections:

1. Place the 50 MHz clock oscillator approximately half-way between the LAN8720I and the RMII MAC in the application. This should ensure relatively matched clock runs to each.
2. Place the series terminations for splitting the 50 MHz clock as close as possible to the clock oscillator in the design.
3. As controlled by the different component placements, the two resultant clock traces should be matched to within 0.10" and have an overall trace length of less than 6.0".

MAC REFCLK Connections:

1. Place the series termination for the MAC supplied 50 MHz clock as close as possible to the MAC in the design.
2. As controlled by the different component placements, the resultant clock trace should be as short as possible.

RBIAS Resistor:

1. The RBIAS resistor (pin 24) should be routed with a short, wide trace. Any noise induced onto this trace may cause system failures. Do not run any traces under the RBIAS resistor.

RMII Interface:

1. The RMII interface on the LAN8720I should be constructed using 68-ohm traces.
2. Similar groups of the RMII interface should be routed together on the PCB. Transmit channel signals should be routed together and separate from Receive channel signals.
3. RMII signals considered critical should be routed on the top layer next to a contiguous, digital ground plane. Slower RMII signals can be routed on the bottom layer of the PCB.
4. As with any high-speed digital design, inter-space and intra-space guidelines between RMII signals should help to improve crosstalk and signal integrity issues.
5. Refer to Figures No. 5 and No. 6 for details on RMII signal routing.

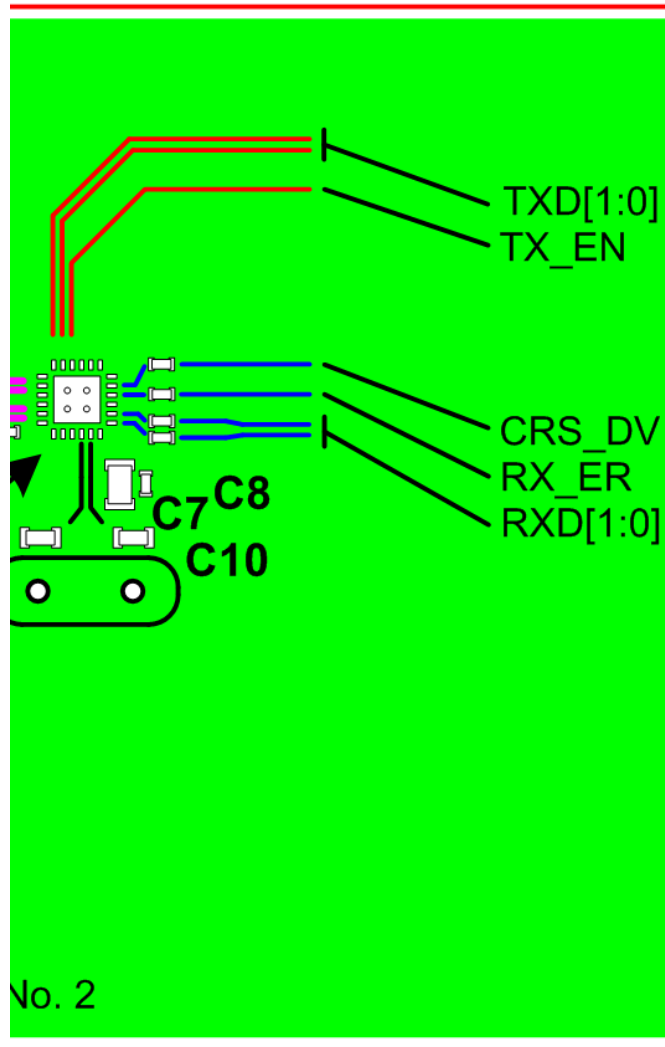


Figure No. 5

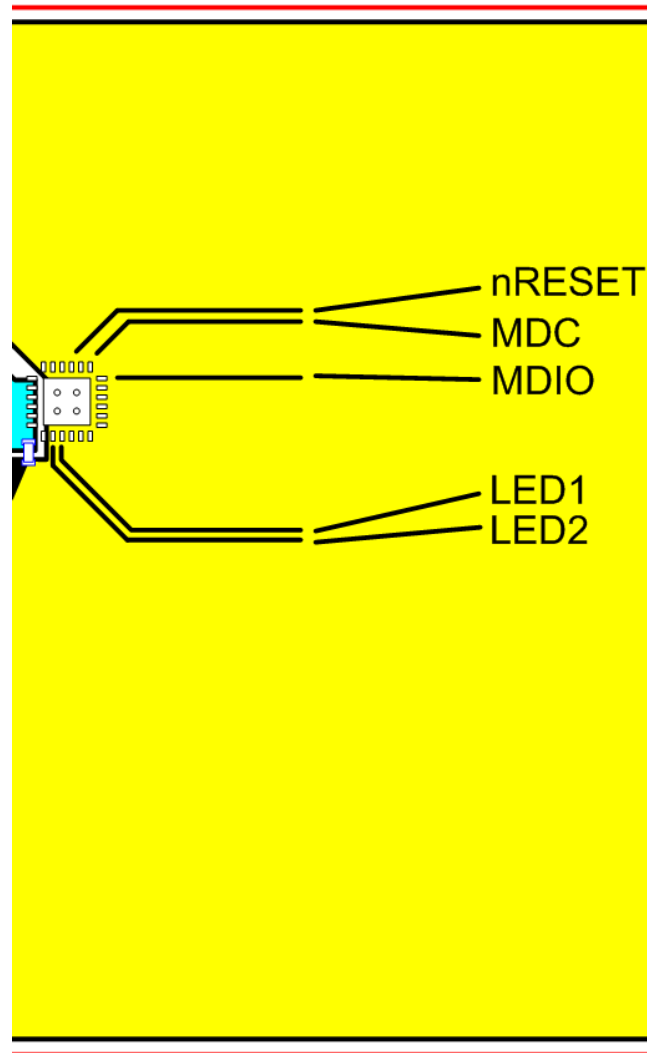


Figure No. 6

RMII Series Terminations:

1. If the designer has elected to use impedance matching terminations in his design, these series resistors should be placed as close as possible to the source of the driving signal.
2. The RMII Series Terminations should be considered critical components. To ensure the best signal integrity and good EMI performance, these critical components should be placed on the component side of the PCB. This will ensure that these components will be referenced to a contiguous ground plane reference on Layer 2 of the design. This will also minimize the use of vias in routing these signals.

Required External Pull-ups:

1. There are no critical routing instructions for the Required External Pull-up connections.

Mode Pins:

1. Since the MODE Pins are shared with the RXD[1..0] and CRS_DV signals of the LAN8720I, any resistor used for termination for the power-on-reset MODE selection, should be placed on the component side of the PCB. This will minimize vias and ensure the reference plane remains constant.
2. Any stub added to the RMII lines due to MODE pin terminations should be kept to a minimum.

Phy Address Pins:

1. Phy Address pin PHYAD0 should also be considered critical. This pin is shared with the RX_ER function of the RMII interface. Any resistor used for termination for the power-on-reset Phy Address selection, should be placed on the component side of the PCB. This will minimize vias and ensure the reference plane remains constant for these three signals.
2. Any stub added to the RMII line due to PHYAD0 termination should be kept to a minimum.

LED Pins:

1. There are no critical routing instructions for the LED Pin connections.

Interrupt Functionality:

1. There are no critical routing instructions for the Interrupt connection.

Miscellaneous:

1. SMSC recommends utilizing at least a four-layer design for boards for the LAN8720I QFN device. The design engineer should be aware, however, as tighter EMC standards are applied to his product and as faster signal rates are utilized by his design, the product design may benefit by utilizing up to eight layers for the PCB construction.
2. As with any high-speed design, the use of series resistors and AC terminations is very application dependant. Buffer impedances should be anticipated and series resistors added to ensure that the board impedance matches the driver. Any critical clock lines should be evaluated for the need for AC terminations. Prototype validation will confirm the optimum value for any series and/or AC terminations.
3. Bulk capacitors for each power plane should be routed immediately into power planes with traces as short as possible and as wide as possible.
4. Following these guidelines and other general design rules in PCB construction should ensure a clean operating system.
5. Trace impedance depends upon many variables (PCB construction, trace width, trace spacing, etc.). The electrical engineer needs to work with the PCB designer to determine all these variables.

No Planes or Traces Underneath Two
Differential Pairs in This Area

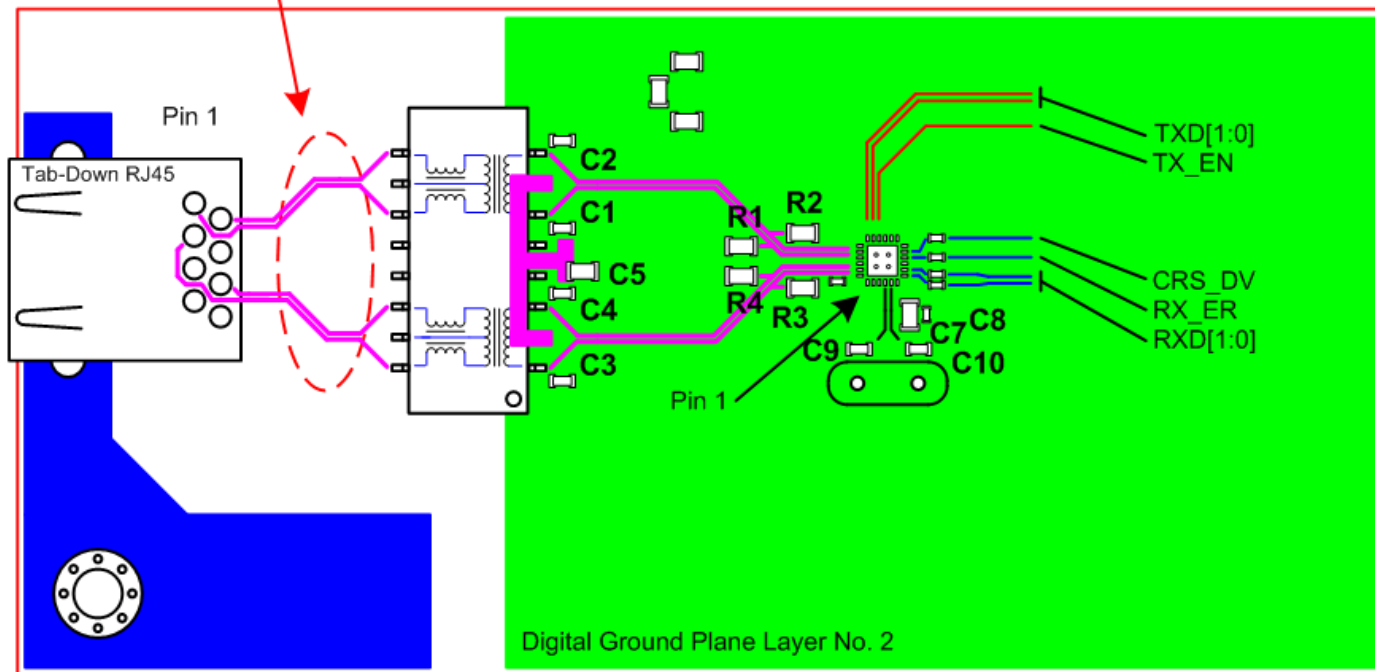


Figure No. 7

No Planes or Traces Underneath Two
Differential Pairs in This Area

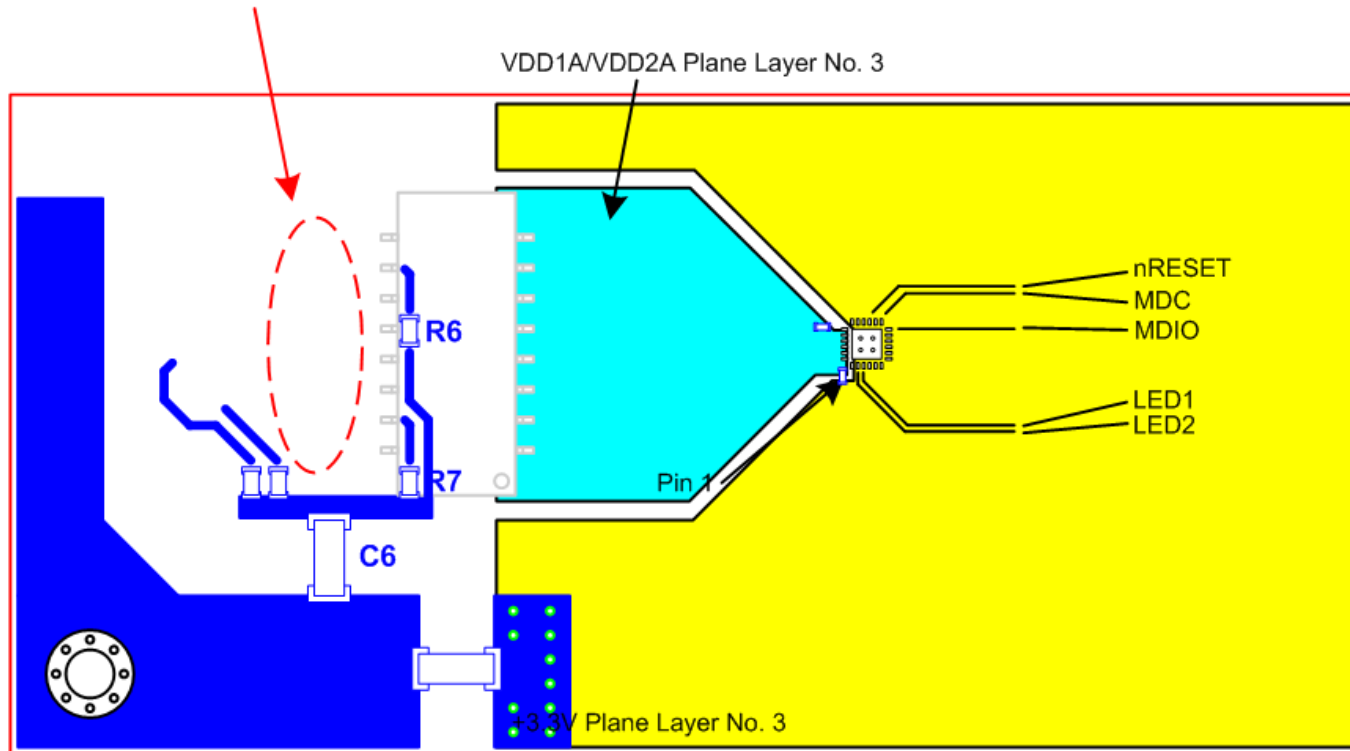


Figure No. 8